

---

**EE 254**

# **Electronic Instrumentation**

**Dr. Tharindu Weerakoon**

Dept. of Electrical and Electronic Engineering

*Faculty of Engineering, University of Peradeniya*

---

***Lecture Note #02***

# Content (Brief)

## 1. Operational Amplifiers

### ✧✧ Ideal Op-Amps

- ✧ Open-loop gain
- ✧ Input resistance
- ✧ Output resistance

### ✧✧ Characteristics of Real Op-Amps

- ✧ Open-loop transfer function
- ✧ Voltage gains
- ✧ Bandwidth
- ✧ Slew rate
- ✧ Power bandwidth
- ✧ Clipping
- ✧ Offset voltages and currents
- ✧ Rejection ratios

# Characteristics of Real Op-Amps

- ✿ Open loop transfer function
- ✿ Voltage gains
- ✿ Bandwidth
- ✿ Slew rate
- ✿ Power bandwidth
- ✿ Clipping
- ✿ Offset voltages and currents
- ✿ Rejection ratios

# Electrical Characteristics

(VCC = 15V, VEE = - 15V. TA = 25 °C, unless otherwise specified)

| Parameter                             |           | Symbol              | Conditions  | KA741/KA741I                              |      |      | Unit |
|---------------------------------------|-----------|---------------------|---|---|------|------|------|
|                                       |           |                     |   | Min.                                      | Typ. | Max. |      |
| Input Offset Voltage                  |           | V <sub>IO</sub>     | R <sub>S</sub> ≤ 10KΩ                             | -   | 2.0  | 6.0  | mV   |
|                                       |           |                     | R <sub>S</sub> ≤ 50Ω                              | -   | -    | -    |      |
| Input Offset Voltage Adjustment Range |           | V <sub>IO(R)</sub>  | VCC = ±20V  | -   | ±15  | -    | mV   |
| Input Offset Current                  |           | I <sub>IO</sub>     | -   | -   | 20   | 200  | nA   |
| Input Bias Current                    |           | I <sub>BIAS</sub>   | -   | -   | 80   | 500  | nA   |
| Input Resistance (Note1)              |           | R <sub>I</sub>      | VCC = ±20V  | 0.3                                       | 2.0  | -    | MΩ   |
| Input Voltage Range                   |           | V <sub>I(R)</sub>   | -   | ±12                                       | ±13  | -    | V    |
| Large Signal Voltage Gain             |           | G <sub>V</sub>      | R <sub>L</sub> ≥ 2KΩ                              | VCC = ±20V,<br>V <sub>O(P-P)</sub> = ±15V | -    | -    | V/mV |
|                                       |           |                     |   | VCC = ±15V,<br>V <sub>O(P-P)</sub> = ±10V | 20   | 200  |      |
| Output Short Circuit Current          |           | I <sub>SC</sub>     | -   | -   | 25   | -    | mA   |
| Output Voltage Swing                  |           | V <sub>O(P-P)</sub> | VCC = ±20V  | R <sub>L</sub> ≥ 10KΩ                     | -    | -    | V    |
|                                       |           |                     |   | R <sub>L</sub> ≥ 2KΩ                      | -    | -    |      |
|                                       |           |                     | VCC = ±15V  | R <sub>L</sub> ≥ 10KΩ                     | ±12  | ±14  |      |
|                                       |           |                     |   | R <sub>L</sub> ≥ 2KΩ                      | ±10  | ±13  |      |
| Common Mode Rejection Ratio           |           | CMRR                | R <sub>S</sub> ≤ 10KΩ, V <sub>CM</sub> = ±12V     | 70  | 90   | -    | dB   |
|                                       |           |                     | R <sub>S</sub> ≤ 50Ω, V <sub>CM</sub> = ±12V      | -   | -    | -    |      |
| Power Supply Rejection Ratio          |           | PSRR                | VCC = ±15V to VCC = ±15V<br>R <sub>S</sub> ≤ 50Ω  | -   | -    | -    | dB   |
|                                       |           |                     | VCC = ±15V to VCC = ±15V<br>R <sub>S</sub> ≤ 10KΩ | 77  | 96   | -    |      |
| Transient Response                    | Rise Time | T <sub>R</sub>      | Unity Gain  | -   | 0.3  | -    | μs   |
|                                       | Overshoot | OS                  |   | -   | 10   | -    | %    |
| Bandwidth                             |           | BW                  | -   | -   | -    | -    | MHz  |
| Slew Rate                             |           | SR                  | Unity Gain  | -   | 0.5  | -    | V/μs |
| Supply Current                        |           | I <sub>CC</sub>     | R <sub>L</sub> = ∞Ω                               | -   | 1.5  | 2.8  | mA   |
| Power Consumption                     |           | P <sub>C</sub>      | VCC = ±20V  | -   | -    | -    | mW   |
|                                       |           |                     | VCC = ±15V  | -   | 50   | 85   |      |

# CMRR (Common Mode Rejection Ratio)

## Electrical Characteristics


( $V_{CC} = 15V$ ,  $V_{EE} = -15V$ ,  $T_A = 25^\circ C$ , unless otherwise specified)

| Parameter                             | Symbol       | Conditions  | KA741/KA741I |          |      | Unit       |
|---------------------------------------|--------------|---|--------------|----------|------|------------|
|                                       |              |   | Min.         | Typ.     | Max. |            |
| Input Offset Voltage                  | $V_{IO}$     | $R_S \leq 10K\Omega$  | -            | 2.0      | 6.0  | mV         |
|                                       |              | $R_S \leq 50\Omega$   | -            | -        | -    |            |
| Input Offset Voltage Adjustment Range | $V_{IO(R)}$  | $V_{CC} = \pm 20V$  | -            | $\pm 15$ | -    | mV         |
| Input Offset Current                  | $I_{IO}$     | -   | -            | 20       | 200  | nA         |
| Input Bias Current                    | $I_{BIAS}$   | -   | -            | 80       | 500  | nA         |
| Input Resistance (Note1)              | $R_i$        | $V_{CC} = \pm 20V$  | 0.3          | 2.0      | -    | M $\Omega$ |
| Input Voltage Range                   | $V_{I(R)}$   | -   | $\pm 12$     | $\pm 13$ | -    | V          |
| Large Signal Voltage Gain             | $G_v$        | $R_L \geq 2K\Omega$<br>$V_{CC} = \pm 20V$ ,<br>$V_{O(P-P)} = \pm 15V$ | -            | -        | -    | V/mV       |
|                                       |              | $V_{CC} = \pm 15V$ ,<br>$V_{O(P-P)} = \pm 10V$                        | 20           | 200      | -    |            |
| Output Short Circuit Current          | $I_{SC}$     | -   | -            | 25       | -    | mA         |
| Output Voltage Swing                  | $V_{O(P-P)}$ | $V_{CC} = \pm 20V$<br>$R_L \geq 10K\Omega$                            | -            | -        | -    | V          |
|                                       |              | $R_L \geq 2K\Omega$   | -            | -        | -    |            |
|                                       |              | $V_{CC} = \pm 15V$<br>$R_L \geq 10K\Omega$                            | $\pm 12$     | $\pm 14$ | -    |            |
|                                       |              | $R_L \geq 2K\Omega$   | $\pm 10$     | $\pm 13$ | -    |            |
| Common Mode Rejection Ratio           | CMRR         | $R_S \leq 10K\Omega$ , $V_{CM} = \pm 12V$                             | 70           | 90       | -    | dB         |
|                                       |              | $R_S \leq 50\Omega$ , $V_{CM} = \pm 12V$                              | -            | -        | -    |            |
| Power Supply Rejection Ratio          | PSRR         | $V_{CC} = \pm 15V$ to $V_{CC} = \pm 15V$<br>$R_S \leq 50\Omega$       | -            | -        | -    | dB         |
|                                       |              | $V_{CC} = \pm 15V$ to $V_{CC} = \pm 15V$<br>$R_S \leq 10K\Omega$      | 77           | 96       | -    |            |
| Transient Response                    | Rise Time    | Unity Gain  | -            | 0.3      | -    | $\mu s$    |
|                                       | Overshoot    |   | -            | 10       | -    | %          |
| Bandwidth                             | BW           | -   | -            | -        | -    | MHz        |
| Slew Rate                             | SR           | Unity Gain  | -            | 0.5      | -    | V/ $\mu s$ |
| Supply Current                        | $I_{CC}$     | $R_L = \infty\Omega$  | -            | 1.5      | 2.8  | mA         |
| Power Consumption                     | PC           | $V_{CC} = \pm 20V$  | -            | -        | -    | mW         |
|                                       |              | $V_{CC} = \pm 15V$  | -            | 50       | 85   |            |





# Ground Noise Problem???

☼ How to overcome this issue?

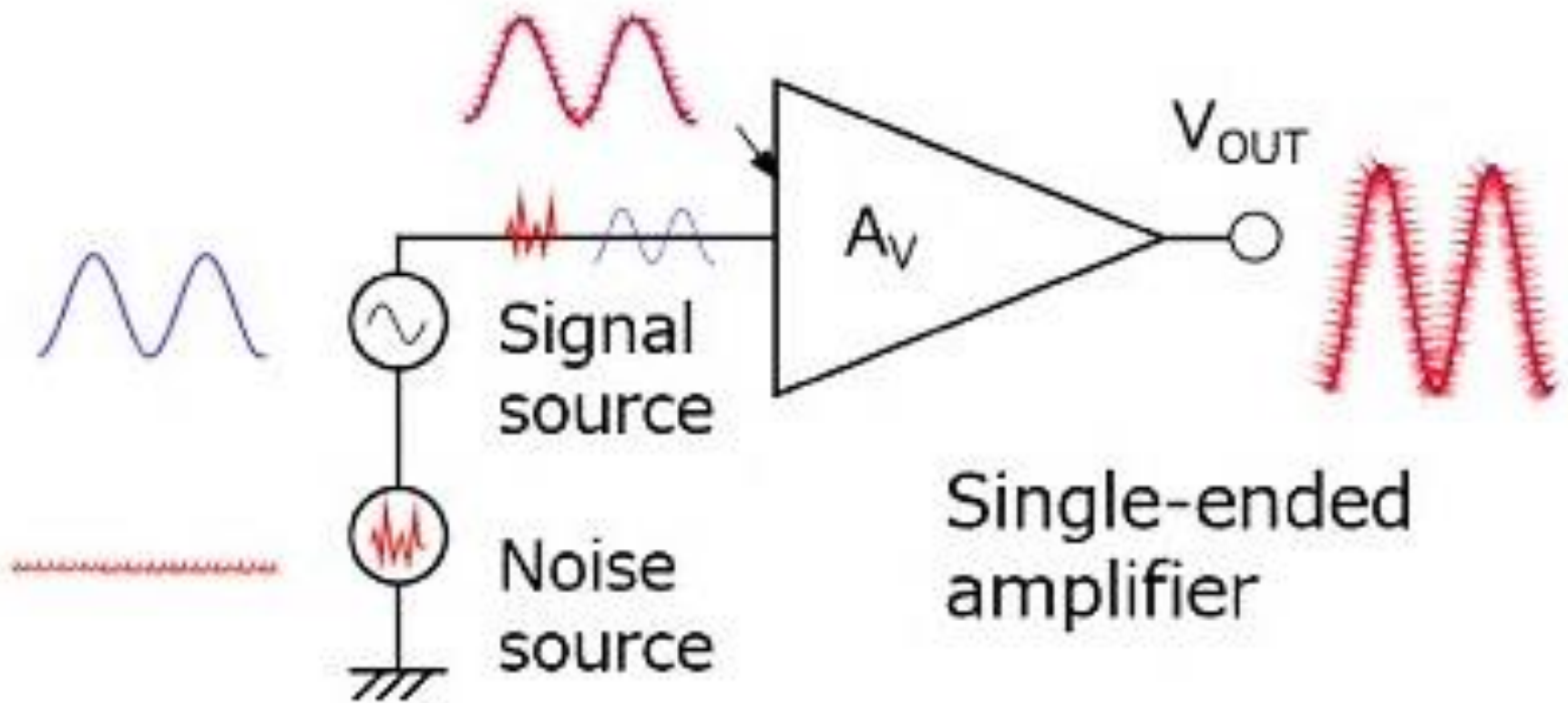

# Ground Noise Problem???

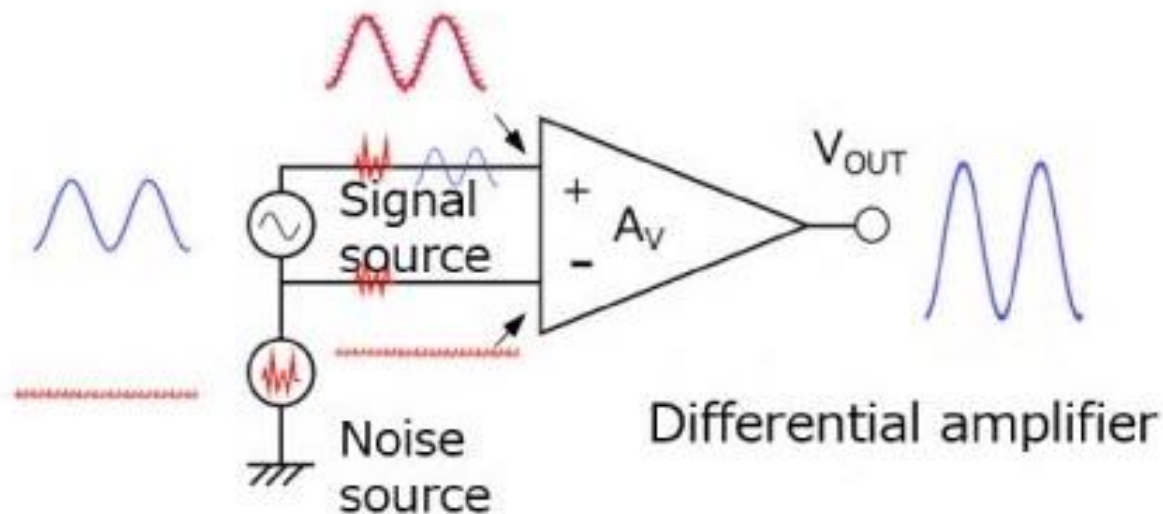
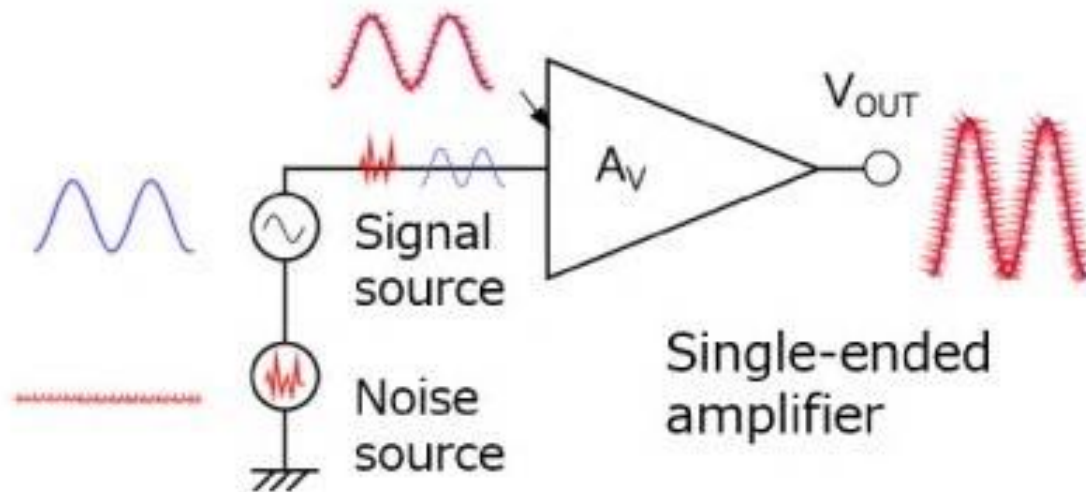





# CMRR (Common Mode Rejection Ratio)

☼ There are two main causes of common-mode noise:

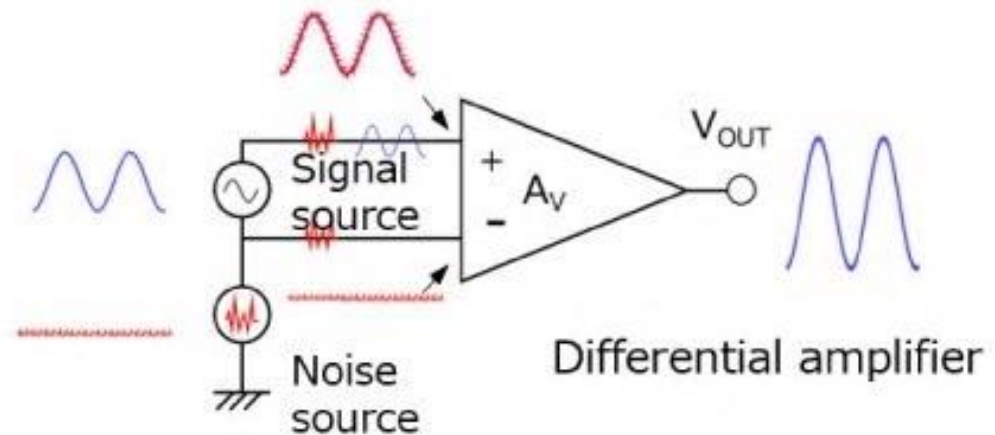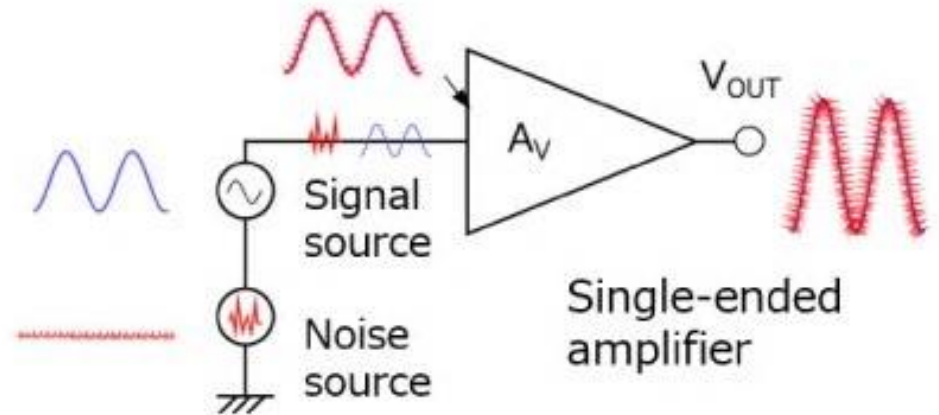1. Noise is generated in the wires and cables, due to electromagnetic induction, etc., and it causes a difference in potential (i.e., noise) between the signal source ground and the circuit ground.
2. Current flowing into the ground of a circuit from another circuit causes a ground potential rise (noise).




# CMRR

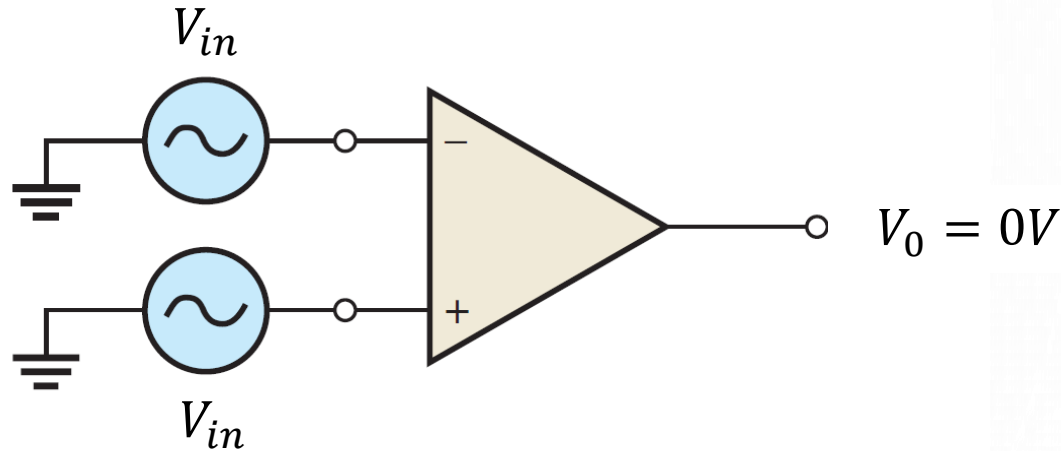

- \* One of the most important specification and Op-Amp parameter.
- \* Unwanted signals (noise) appearing with the same polarity on both input lines are essentially cancelled by the op-amp and do not appear on the output.
- \* i.e. two input signals will cancel and resulting a zero output voltage.
- \* This action is called ***common-mode rejection***. The parameter is called as CMRR (common-mode rejection ratio).

# CMRR

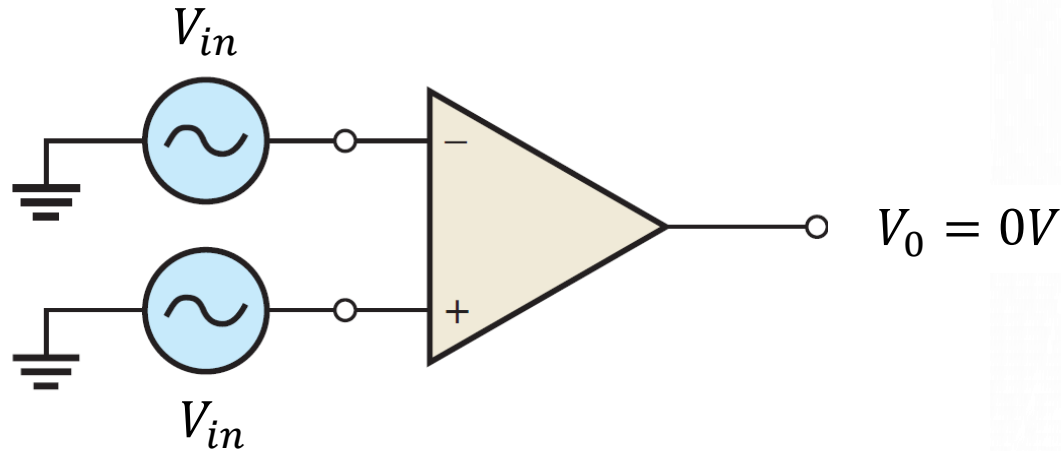

- \*❖ **Ideally**, an op-amp provides a **very high gain for differential-mode signals** and **zero gain for common-mode signals**.
- \*❖ If unwanted signals appear commonly on both op-amp inputs, output will not be zero.
- \*❖ Common-mode signals (noise) are generally the result of the radiated energy on the input lines, from adjacent lines, the 50Hz power line or other sources.

# CMRR

- \* **Practical op-amps** have a very small common-mode gain (usually much less than 1), while providing a high open-loop differential voltage gain (usually several thousand).
- \* The higher the open-loop gain ( compared to the common-mode gain), the better the performance of the op-amp in terms of rejection of common-mode signals.
- \* This suggests that a good measure of the op-amp's performance in rejecting unwanted common-mode signals is the ratio of the **open-loop differential voltage gain,  $A_{ol}$** , to the **common-mode gain,  $A_{cm}$** .
- \* The common-mode rejection ratio, CMRR can be calculated as:

$$\text{CMRR} = \frac{A_{ol}}{A_{cm}}$$

# CMRR

- ✿ The higher the CMRR, the better.
- ✿ A very high value of CMRR means that the open-loop gain,  $A_{ol}$ , is high and the common-mode gain,  $A_{cm}$ , is low.
- ✿ The CMRR is often expressed in decibels (dB) as

$$\text{CMRR} = \frac{A_{ol}}{A_{cm}} \qquad \text{CMRR} = 20 \log_{10} \left( \frac{A_{ol}}{A_{cm}} \right)$$

- ✿ The **open-loop voltage gain**,  $A_{ol}$ , of an op-amp is the internal voltage gain of the device and represents the ratio of output voltage to input voltage when there are no external components.
- ✿ The open-loop voltage gain is set entirely by the internal design.  
Open-loop
- ✿ voltage gain can range up to 200,000 (106 dB) and is not a well-controlled parameter. Datasheets often refer to the open-loop voltage gain as the *large-signal voltage gain*.



# CMRR

✿ If CMRR is 100,000, what does it mean?

- ✿ A CMRR of 100,000, for example, means that the desired input signal (differential) is amplified 100,000 times more than the unwanted noise (common-mode).
- ✿ If the amplitudes of the differential input signal and the common-mode noise are equal, the desired signal will appear on the output 100,000 times greater in amplitude than the noise.
- ✿ Thus, the noise or interference has been essentially eliminated.



# Output Voltage Swing ( $V_{O(P-P)}$ )

- ✿ With no input signal, the output of an op-amp is ideally 0 V.
- ✿ This is called the **quiescent output voltage**.
- ✿ When an input signal is applied, the ideal limits of the peak-to-peak output signal are  $\pm V_{CC}$
- ✿ In practice, however, this ideal can be approached but never reached.
- ✿  $V_{O(P-P)}$  varies with the load connected to the op-amp and increases directly with load resistance.
- ✿ For example, from the KA741 datasheet

| Parameter            | Symbol       | Conditions         |                      | KA741/KA741I |          |      | Unit |
|----------------------|--------------|--------------------|----------------------|--------------|----------|------|------|
|                      |              |                    |                      | Min.         | Typ.     | Max. |      |
| Output Voltage Swing | $V_{O(P-P)}$ | $V_{CC} = \pm 20V$ | $R_L \geq 10K\Omega$ | -            | -        | -    | V    |
|                      |              |                    | $R_L \geq 2K\Omega$  | -            | -        | -    |      |
|                      |              | $V_{CC} = \pm 15V$ | $R_L \geq 10K\Omega$ | $\pm 12$     | $\pm 14$ | -    |      |
|                      |              |                    | $R_L \geq 2K\Omega$  | $\pm 10$     | $\pm 13$ | -    |      |

# Output Voltage Swing ( $V_{O(P-P)}$ )

- Some op-amps do not use both positive and negative supply voltages.
- One example is when a single dc voltage source is used to power an op-amp that drives an analog-to-digital converter.
- In this case, the op-amp output is designed to operate between ground and a full scale output that is near (or at) the positive supply voltage.
- Op-amps that operate on a single supply use the terminology  $V_{OH}$  and  $V_{OL}$  to specify the maximum and minimum output voltage. (Note that these are not the same as the digital definitions of  $V_{OL}$  and  $V_{OH}$ .)

# Input Offset Voltage


- ✿ The ideal op-amp produces zero volts out for zero volts in.
- ✿ In a practical op-amp, however, a small dc voltage,  $V_{OUT}(\text{error})$ , appears at the output when no differential input voltage is applied. Its primary cause is a slight mismatch of the base-emitter voltages of the differential amplifier input stage of an op-amp.
- ✿ As specified on an op-amp datasheet, the input offset voltage,  $V_{OS}$ , is the differential dc voltage required between the inputs to force the output to zero volts.
- ✿ Typical values of input offset voltage are in the range of 2 mV or less. In the ideal case, it is 0 V.

| Parameter            | Symbol   | Conditions           | KA741/KA741I |      |      | Unit |
|----------------------|----------|----------------------|--------------|------|------|------|
|                      |          |                      | Min.         | Typ. | Max. |      |
| Input Offset Voltage | $V_{IO}$ | $R_S \leq 10K\Omega$ | -            | 2.0  | 6.0  | mV   |
|                      |          | $R_S \leq 50\Omega$  | -            | -    | -    |      |

# Input Bias Current


- ❁ You have seen that the input terminals of a bipolar differential amplifier are the transistor bases and, therefore, the input currents are the base currents.
- ❁ The input bias current is the dc current required by the inputs of the amplifier to properly operate the first stage.
- ❁ By definition, the input bias current is the average of both input currents and is calculated as follows:

$$I_{BIAS} = \frac{I_1 + I_2}{2}$$

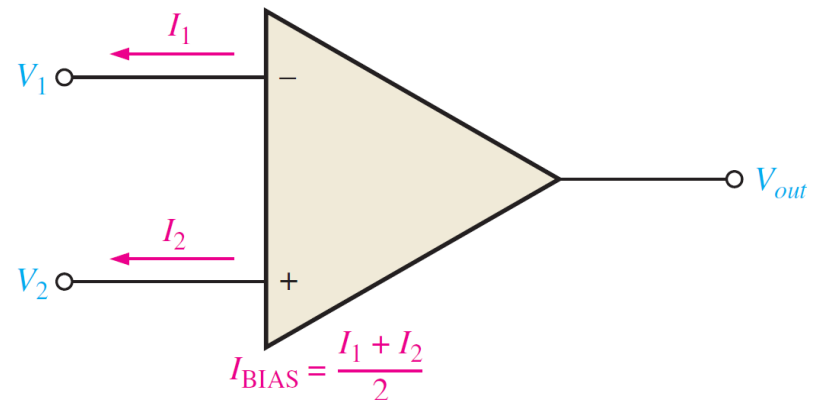

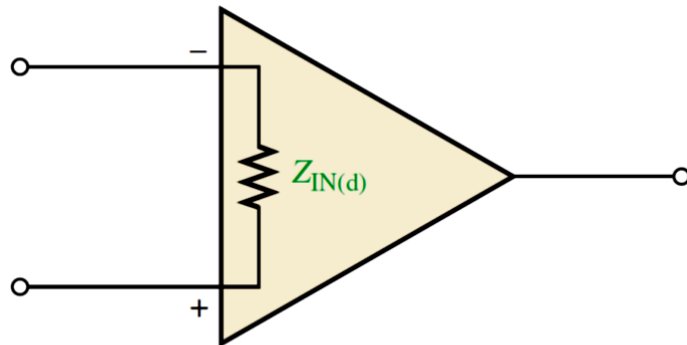
# Input Impedance

- ❁ Two basic ways of specifying the input impedance of an op-amp are the differential and the common mode.
- ❁ The differential input impedance is the total resistance between the inverting and the noninverting inputs (a).
- ❁ Differential impedance is measured by determining the change in bias current for a given change in differential input voltage.
- ❁ The common-mode input impedance is the resistance between each input and ground and is measured by determining the change in bias current for a given change in common-mode input voltage (b).



(a) Differential input impedance

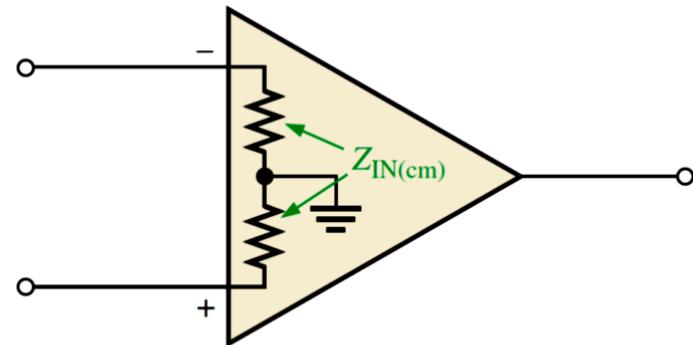

(b) Common-mode input impedance

# Input Offset Current


- ✿ Ideally, the two input bias currents are equal, and thus their difference is zero.
- ✿ In a practical op-amp, however, the bias currents are not exactly equal.
- ✿ The input offset current,  $I_{OS}$ , is the difference of the input bias currents, expressed as an absolute value.

$$I_{OS} = |I_1 - I_2|$$



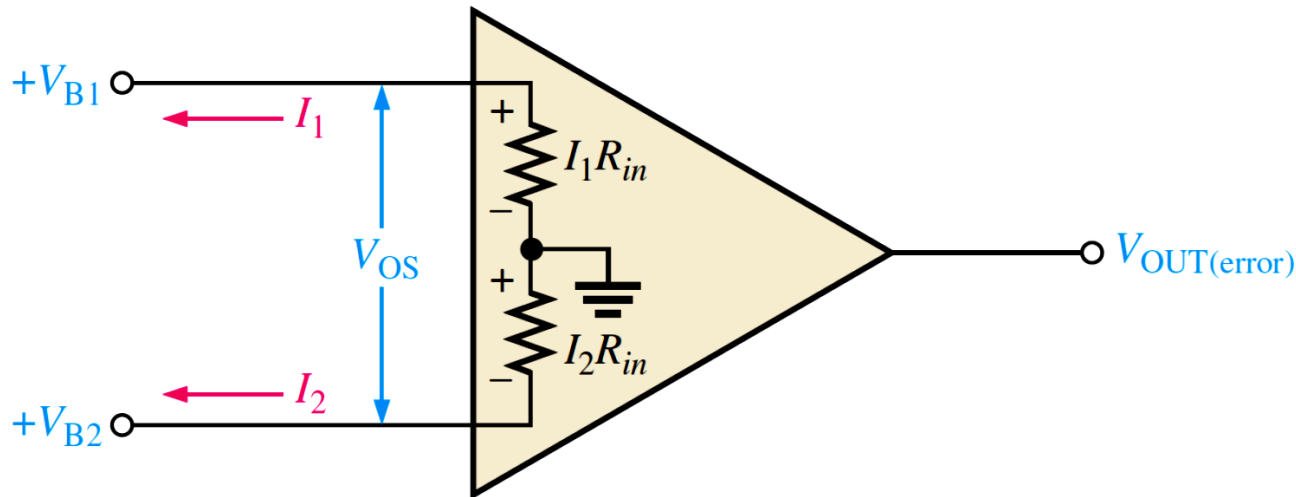
# Input Offset Current

- Actual magnitudes of offset current are usually at least an order of magnitude (ten times) less than the bias current.
- In many applications, the offset current can be neglected.
- However, high-gain, high-input impedance amplifiers should have as little  $I_{OS}$  as possible because the difference in currents through large input resistances develops a substantial offset voltage, as shown in Figure



# Input Offset Current

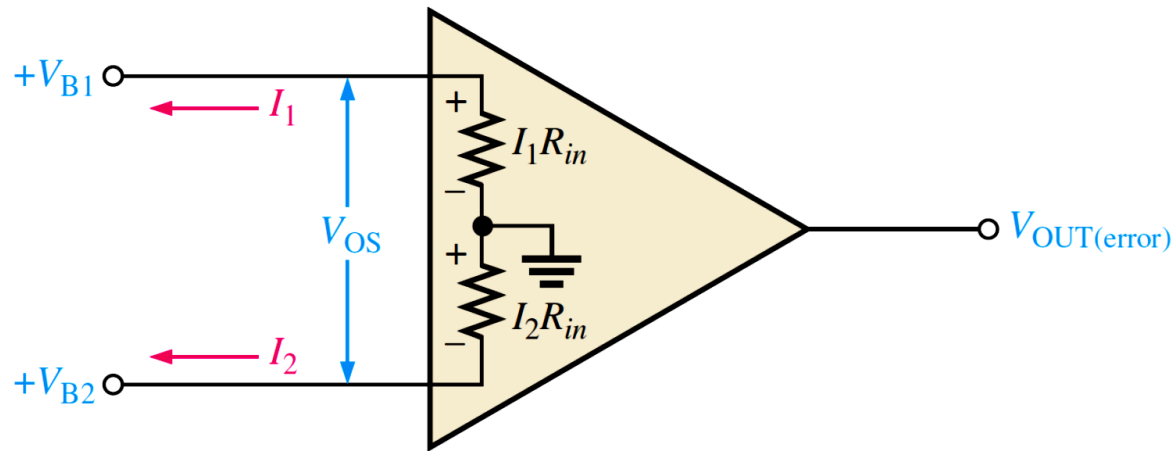

- ✿ The offset voltage developed by the input offset current is

$$V_{OS} = I_1 R_{in} - I_2 R_{in} = (I_1 - I_2) R_{in}$$


$$V_{OS} = I_{OS} R_{in}$$

- ✿ The error created by  $I_{OS}$  is amplified by the gain  $A_v$  of the op-amp and appears in the output as

$$V_{OUT(error)} = A_v I_{OS} R_{in}$$

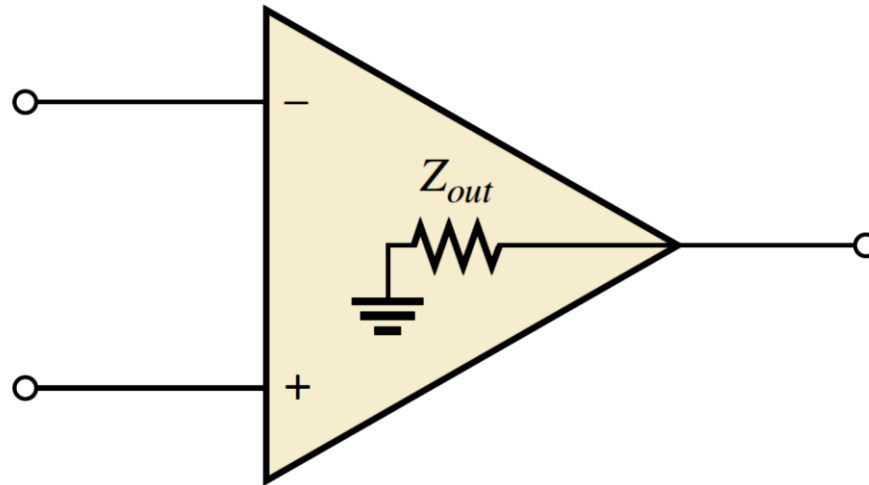
# Output Impedance

- ✿ The *output impedance* is the resistance viewed from the output terminal of the op-amp.


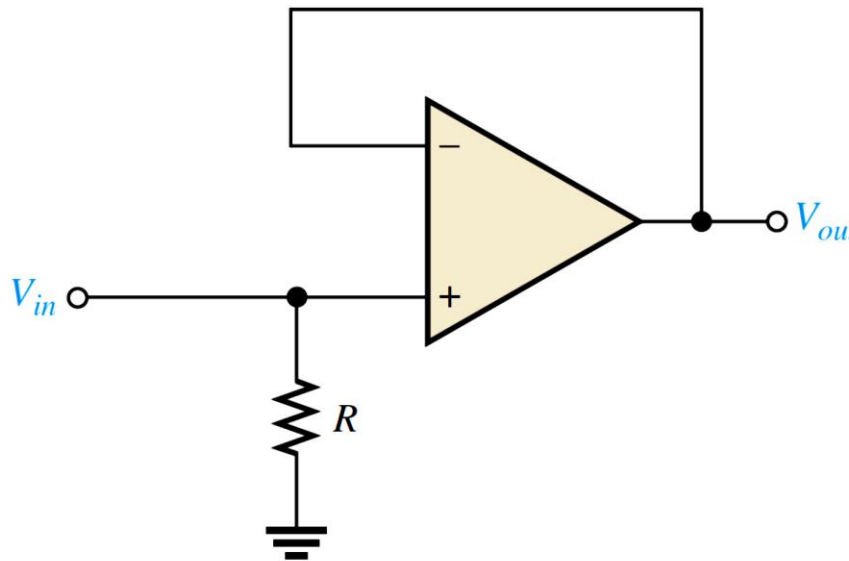
# Slew Rate


- ❁ The maximum rate of change of the output voltage in response to a step input voltage is the slew rate of an op-amp.
- ❁ The slew rate is dependent upon the high-frequency response of the amplifier stages within the op-amp.
- ❁ Slew rate is measured with an op-amp connected as shown in Figure.



(a) Test circuit
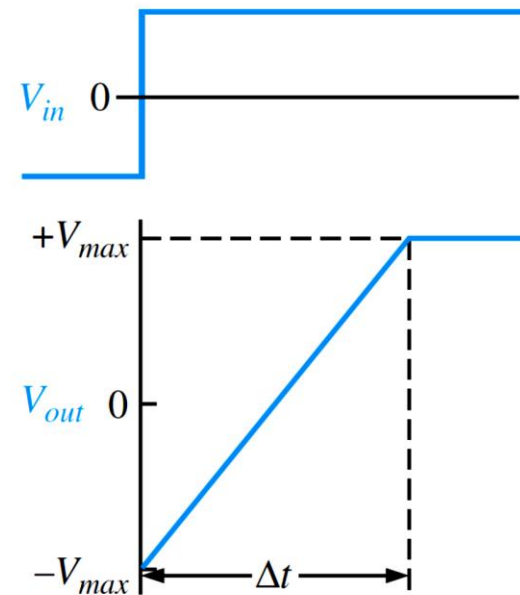
# Slew Rate

- ✿ It gives a worst-case (slowest) slew rate. Recall that the high frequency components of a voltage step are contained in the rising edge and that the upper critical frequency of an amplifier limits its response to a step input.
- ✿ For a step input, the slope on the output is inversely proportional to the upper critical frequency.
- ✿ Slope increases as upper critical frequency decreases.
- ✿ A pulse is applied to the input and the resulting ideal output voltage is indicated in Figure



(b) Step input voltage and the resulting output voltage

# Slew Rate

- ✿ The width of the input pulse must be sufficient to allow the output to “slew” from its lower limit to its upper limit.
- ✿ A certain time interval  $\Delta t$ , is required for the output voltage to go from its lower limit  $-V_{max}$  to its upper limit  $+V_{max}$  once the input step is applied.


- ✿ The slew rate is expressed as

$$\text{Slew rate} = \frac{\Delta V_{out}}{\Delta t}$$

- ✿ Where;

$$\Delta V_{out} = +V_{max} - (-V_{max})$$

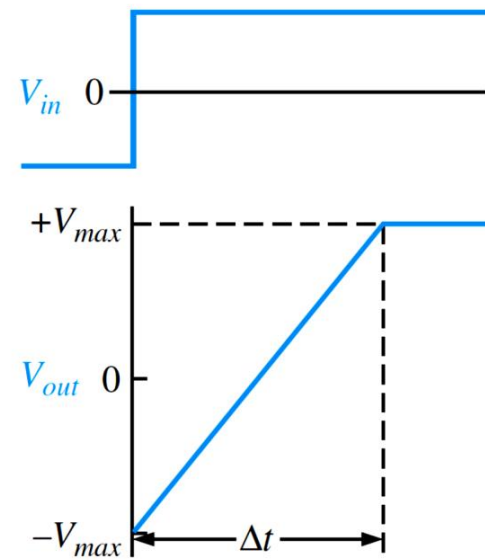- ✿ The unit of slew rate is volts per microsecond ( $V/\mu s$ ).



(b) Step input voltage and the resulting output voltage



# Comparison of Op-Amp Parameters

- ❁ As you can see from the table, there is a wide difference in certain specifications.
- ❁ All designs involve certain compromises, so in order for designers to optimize one parameter, they must often sacrifice another parameter.
- ❁ Choosing an op-amp for a particular application depends on which parameters are important to optimize.
- ❁ Parameters depend on the conditions for which they are measured.
- ❁ For details on any of these specifications, consult the datasheet.

# Comparison of Op-Amp Parameters

| OP-AMP  | CMRR<br>(dB)<br>(TYP) | OPEN-<br>LOOP<br>GAIN<br>(dB)<br>(TYP) | GAIN-<br>BANDWIDTH<br>PRODUCT<br>(MHz)<br>(TYP) | INPUT<br>OFFSET<br>VOLTAGE<br>(mV)<br>(MAX) | INPUT<br>BIAS<br>CURRENT<br>(nA)<br>(MAX) | SLEW<br>RATE<br>(V/μs)<br>(TYP) | COMMENT  | <sup>1</sup> Depends on gain; gain = 10 is shown<br><sup>2</sup> Depends on gain; gain = 2 is shown<br><sup>3</sup> Small signal |
|---------|-----------------------|--|---|---|---|---------------------------------|--|--|
|         |                       |  |   |   |   |                                 |  |  |
| AD8009  | 50                    | N/A                                    | 320 <sup>1</sup>                                | 5   | 150                                       | 5500                            | Extremely fast, low distortion, uses current feedback  |  |
| AD8055  | 82                    | 71                                     |   | 5   | 1200                                      | 1400                            | Low noise, fast, wide bandwidth, gain flatness 0.1 dB, video driver                              |  |
| ADA4891 | 68                    | 90 <sup>2</sup>                        |   | 2500  | 0.002                                     | 170                             | CMOS-extremely low bias current, very fast, useful as video amplifier                            |  |
| ADA4092 | 85                    | 118                                    | 1.3   | 0.2   | 50  | 0.4                             | Single supply (2.7 V to 36 V) or two supply operation, low power                                 |  |
| FAN4931 | 73                    | 102                                    | 4   | 6   | 0.005                                     | 3                               | Low cost CMOS, low power, output swings to within 10 mV of rail, extremely high input resistance |  |
| FHP3130 | 95                    | 100                                    | 60  | 1   | 1800                                      | 110                             | High current output (to 100 mA)  |  |
| FHP3350 | 90                    | 55                                     | 190   | 1   | 50  | 800                             | High speed; useful as video amp  |  |
| LM741C  | 70                    | 106                                    | 1   | 6   | 500                                       | 0.5                             | General-purpose, overload protection, industry standard  |  |
| LM7171  | 110                   | 90                                     | 100   | 1.5   | 1000                                      | 3600                            | Very fast, high CMRR, useful as an instrumentation amplifier                                     |  |
| LMH6629 | 87                    | 79                                     | 800 <sup>3</sup>                                | 0.15  | 23000                                     | 530                             | Fast, ultra low noise, low voltage   |  |
| OP177   | 130                   | 142                                    |   | 0.01  | 1.5                                       | 0.3                             | Ultra-precision; very high CMRR and stability  |  |
| OPA369  | 114                   | 134                                    | 0.012   | 0.25  | 0.010                                     | 0.005                           | Extremely low power, low voltage, rail-to-rail.  |  |
| OPA378  | 100                   | 110                                    | 0.9   | 0.02  | 0.15                                      | 0.4                             | Precision, very low drift, low noise   |  |
| OPA847  | 110                   | 98                                     | 3900  | 0.1   | 42,000                                    | 950                             | Ultra low-noise, wide bandwidth amplifier, voltage feedback                                      |  |

# Comparison of Op-Amp Parameters

- ✿ There is a wide difference in certain specifications, in the table.
- ✿ All designs involve certain compromises, so in order for designers to optimize one parameter, they must often sacrifice another parameter.
- ✿ Choosing an op-amp for a particular application depends on which parameters are important to optimize.
- ✿ Parameters depend on the conditions for which they are measured.
- ✿ For details on any of these specifications, consult the datasheet.
- ✿ Most available op-amps have three important features: short-circuit protection, no latch-up, and input offset nulling.
- ✿ Short-circuit protection keeps the circuit from being damaged if the output becomes shorted, and the no latch-up feature prevents the op-amp from hanging up in one output state (high or low voltage level) under certain input conditions.
- ✿ Input offset nulling is achieved by an external potentiometer that sets the output voltage at precisely zero with zero input.