

---

**EE 254**

# **Electronic Instrumentation**

**Dr. Tharindu Weerakoon**

Dept. of Electrical and Electronic Engineering

*Faculty of Engineering, University of Peradeniya*

---

***Lecture Note #11***



## 4. Data Converters

- \*\*\* Analogue to Digital (A/D) Conversion (ADC)
- \*\*\* Digital to Analogue (D/A) Conversion (DAC)
- \*\*\* Sample and Hold Circuit

# A/D and D/A Conversion Techniques
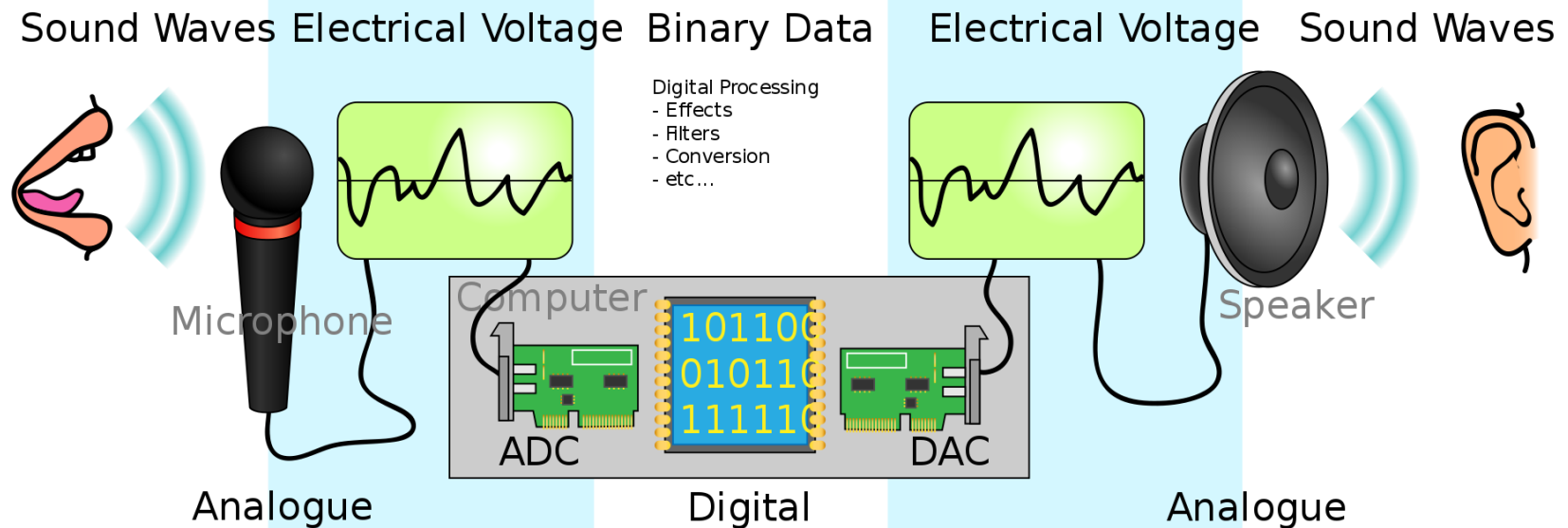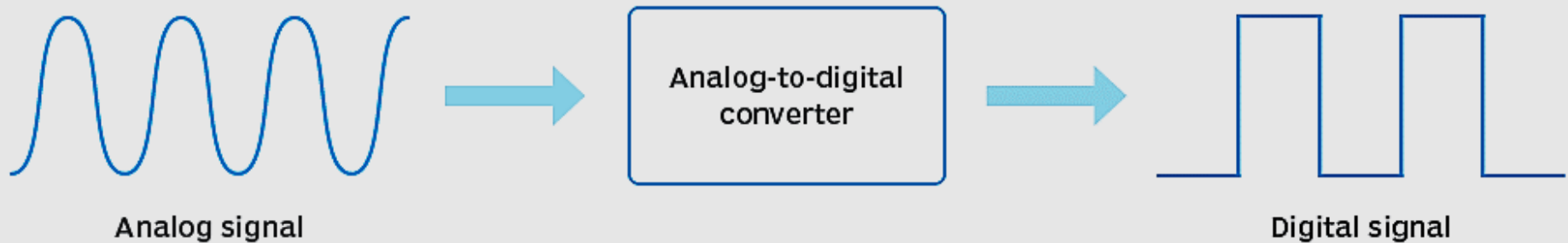
# What and Why ?

- What is data conversion?
- Why data conversion is needed?




# What and Why ?

## 🌀 Analogue to Digital Converter (ADC)

Converts analogue sound into digital signals that can be stored on a computer
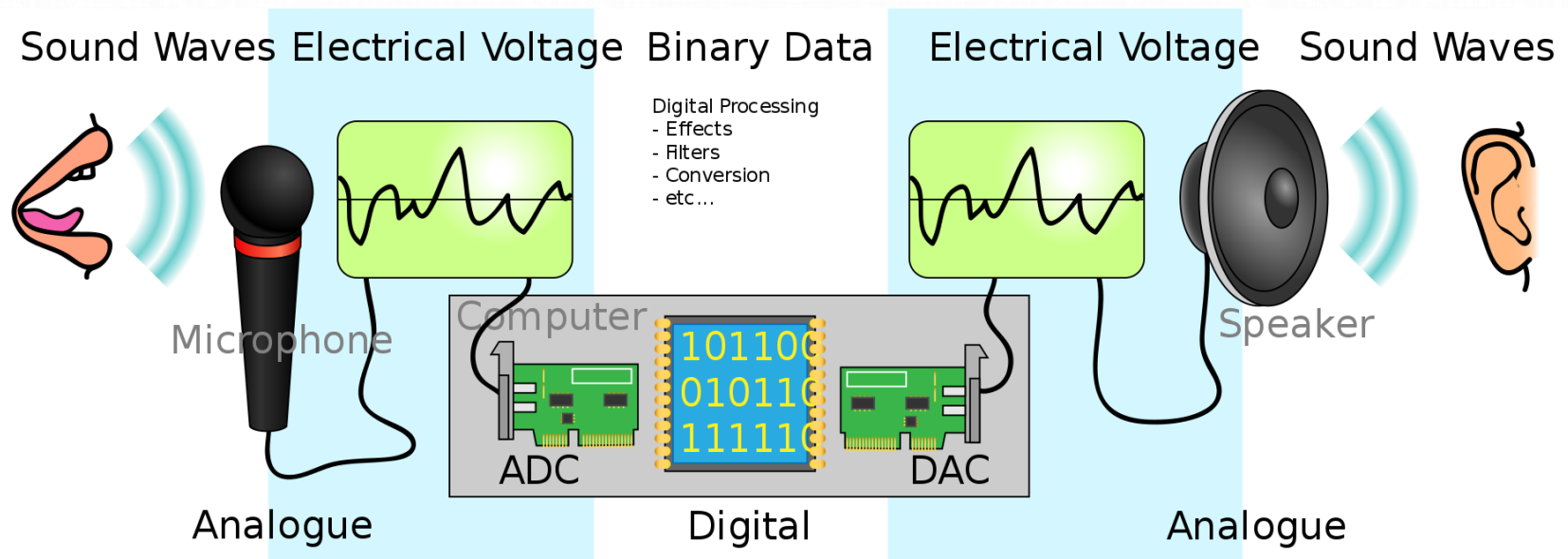
## 🌀 Digital to Analogue Converter (DAC)

Converts digital signals stored on a computer into analogue sound that can be played through devices such as speakers




❁ **fig 1.** The original analogue sound wave is *a continuous set of points*

❁ **fig 2.** ADC converts sound into *digital data*

❁ **fig 3.** DAC converts digital data into *analogue sound*, the analogue wave produced may differ significantly from the original sound wave


fig. 1

 

Conversion A-D




fig. 2

 


Conversion D-A



fig. 3

 

# Basic A/D and D/A Concepts

 

Conversion to an N-bit digital signal:

$$v_D = \frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} + \cdots + \frac{b_N}{2^N}$$


where  $b_1$ ,  $b_2$ , etc. are the bit coefficients that are either a 1 or 0. An analog signal  $v_A$  is applied to the input of the A/D converter.

✿ The bit  $b_1$  is the **most significant bit (MSB)** and the bit  $b_N$  is the **least significant bit (LSB)**.



 
# Analog-to-Digital Conversion Concept

- ✿ Conversion of an analog signal represented by a voltage in the range  $0 \leq v_A \leq 5\text{ V}$  to a 6-bit word digital signal.






# Analog-to-Digital Conversion Concept

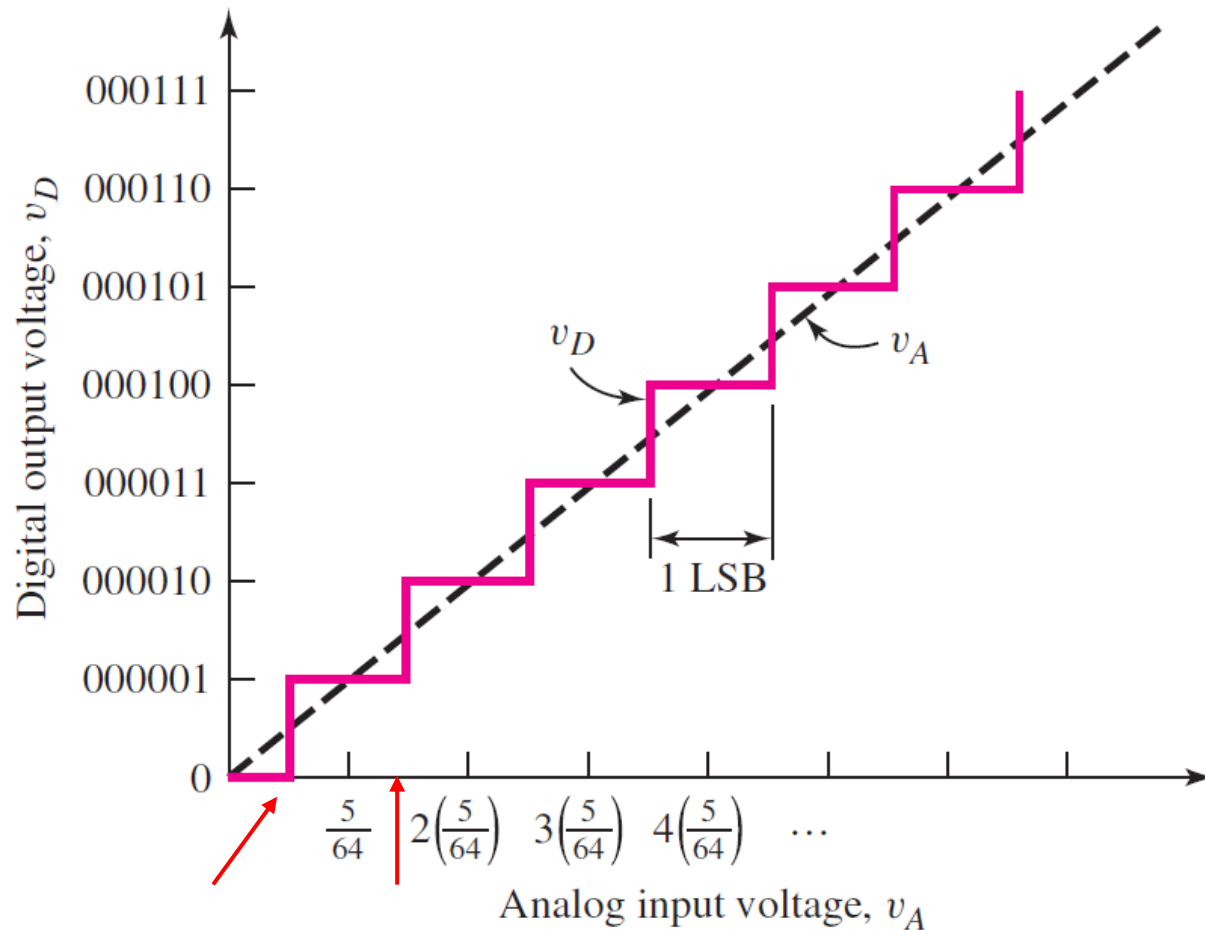

- There is an Quantization error in A/D conversion.
- A larger number of bits can reduce it, but requires a more complex circuit.

# Digital-to-Analog Conversion Concept

 

- ✿  $v'_A$  is in the form of stair steps.
- ✿ Normally,  $v'_A$  is fed through a low-pass filter to smooth out the signal to produce the dotted signal  $v''_A$

# Analogue-to-Digital Converters


1. Parallel or Flash ADC
2. Counting ADC
3. Dual-Slope ADC
4. Successive Approximation A/D Converter
5. Semi-flash ADC
6. Delta-Sigma ADC
7. Pipelined ADC

# Analog-to-Digital Converters

## ① Parallel or Flash A/D

- ✿ Is the simplest in concept.
- ✿ The analog input signal  $v_A$  is applied to seven comparators at the noninverting terminals.
- ✿ A reference voltage is applied to a resistive ladder network.
- ✿ The outputs of the ladder network are applied to the inverting terminals of the comparators.

### 3-bit flash A/D converter

 

# Analog-to-Digital Converters

## ① Parallel or Flash A/D

- ✿ The total resistance in the ladder network is  $8R$ .
- ✿  $V_{REF}/8R$  represents 1 LSB in terms of current.
- ✿ **The smallest output voltage:**


$$v_1 = \frac{V_{REF}}{8R} \left( \frac{R}{2} \right) = \frac{V_{REF}}{16}$$

which represents  $\frac{1}{2}$  LSB.

- ✿ **The second output voltage:**

$$v_2 = \frac{V_{REF}}{8R} \left( \frac{3R}{2} \right) = 3 \left( \frac{V_{REF}}{16} \right)$$


which represents  $1 \frac{1}{2}$  LSB.

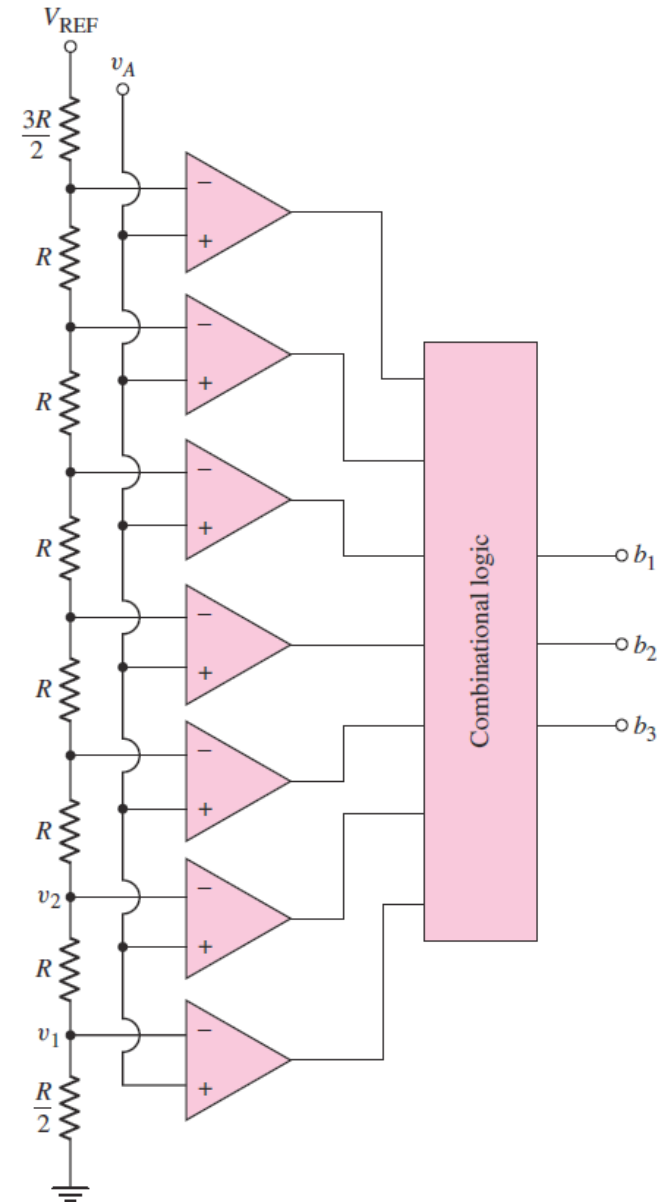

# Analog-to-Digital Converters
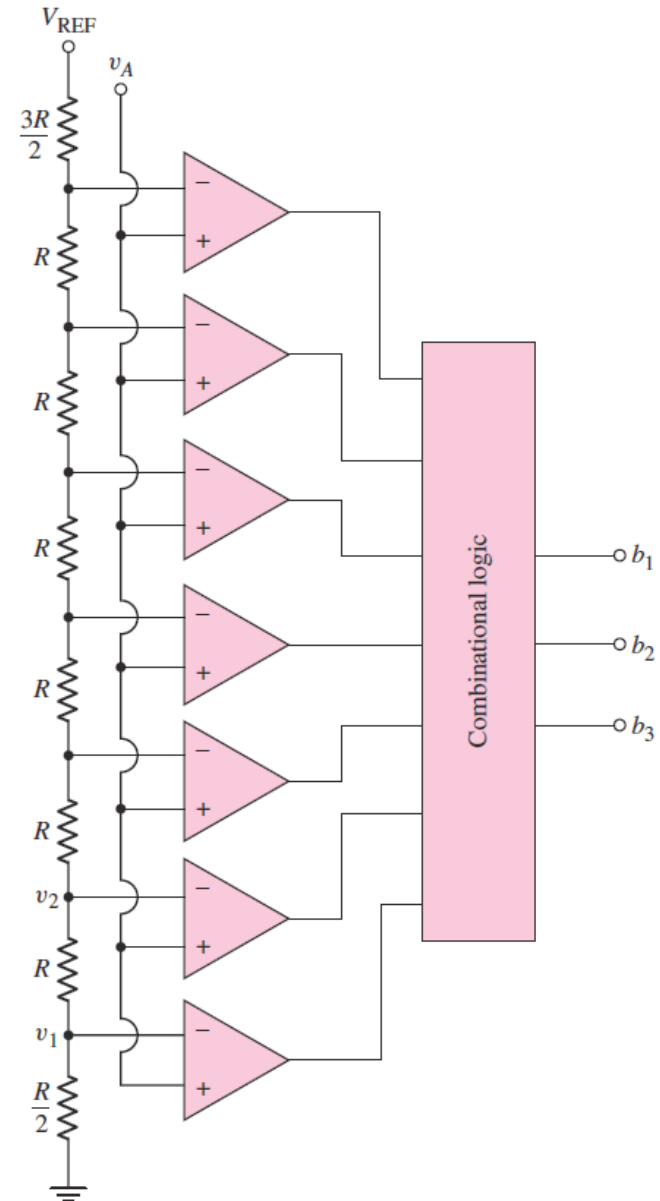
## ① Parallel or Flash A/D


- ✿ If the analog input is  $v_A < \frac{1}{2} \text{ LSB}$ , the output of all comparators will be low.
- ✿ If the analog input is  $\frac{1}{2} \text{ LSB} < v_A < 1 \frac{1}{2} \text{ LSB}$ , the output of the first comparator goes high.
- ✿ As the analog input voltage increases, the outputs of additional comparators go high.
- ✿ The combinational logic network then produces the desired 3-bit output word.



# Analog-to-Digital Converters
 
## ① Parallel or Flash A/D


- ❁ One of the disadvantages of the flash A/D converter is that the number of resistors and comparators increases rapidly as the desired number of output bits increases.
- ❁  $2^N$  resistors and  $2^N - 1$  comparators are required.
- ❁ *Thus, for a 10-bit word, 1024 resistors and 1023 comparators are required.*
- ❁ *However, 10-bit resolution A/D flash converters have been fabricated as ICs.*






# Analog-to-Digital Converters

## ① Parallel or Flash A/D

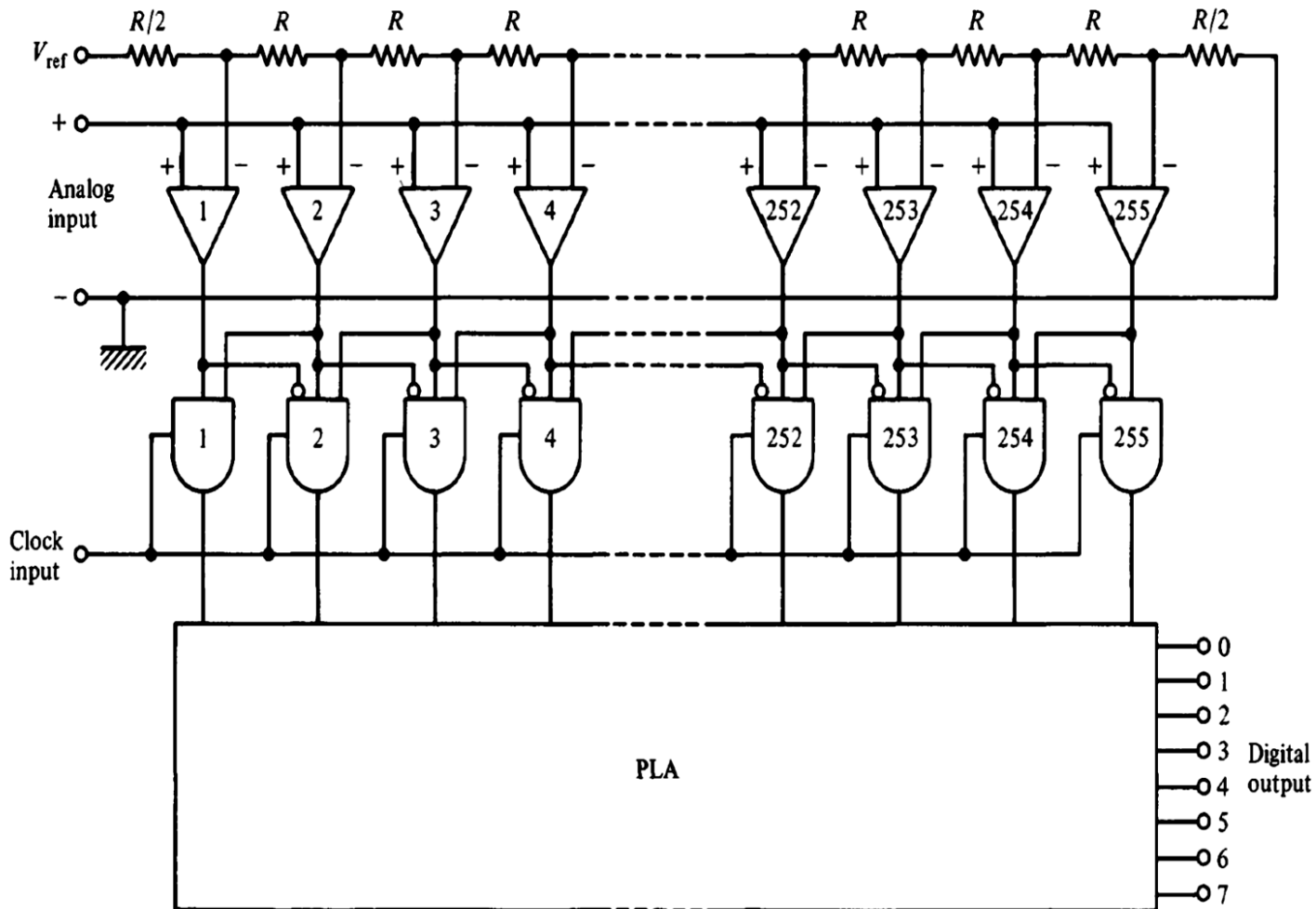

# Analog-to-Digital Converters

## ② Counting A/D

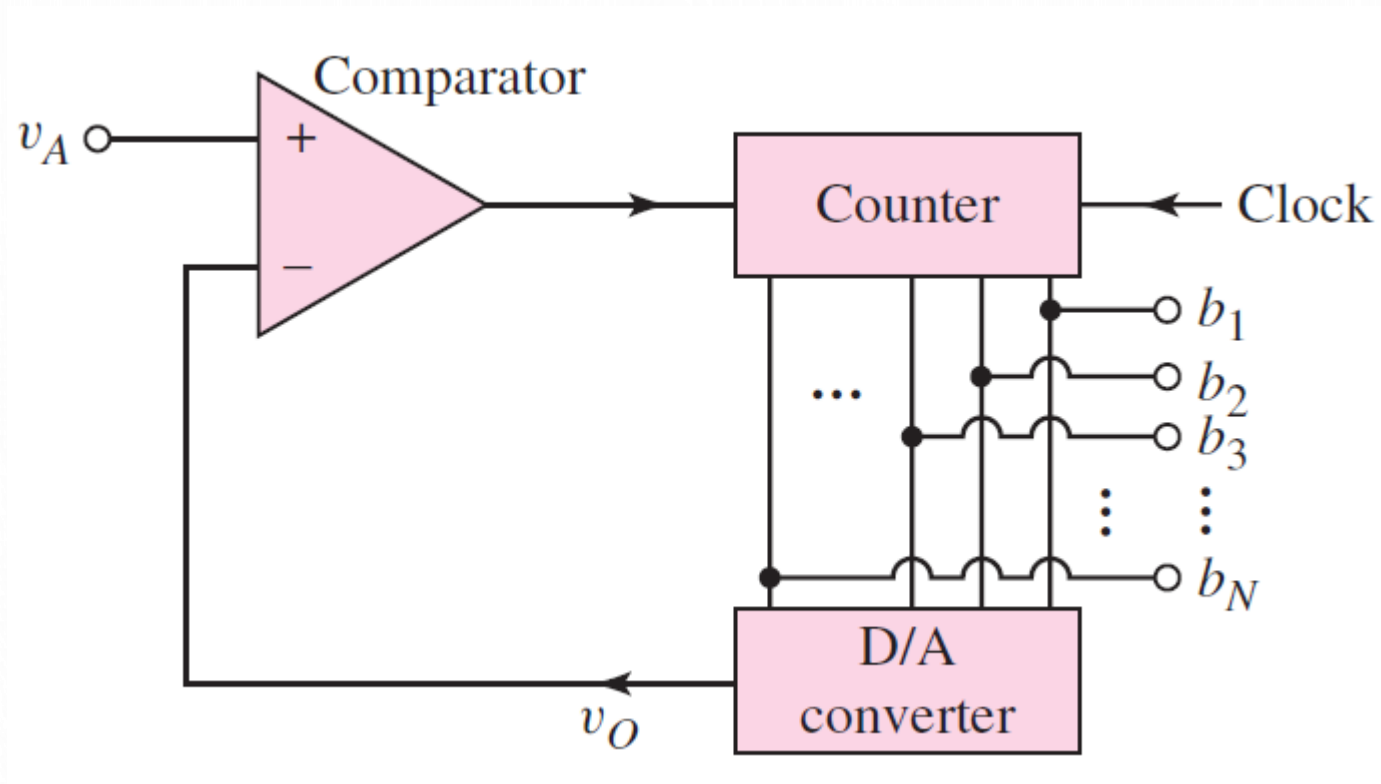


- ✿ This system contains a **comparator**, a **counter**, and a **D/A converter** in a feedback configuration.
- ✿ *There is an additional control circuit which is not shown for simplicity.*

# Analog-to-Digital Converters
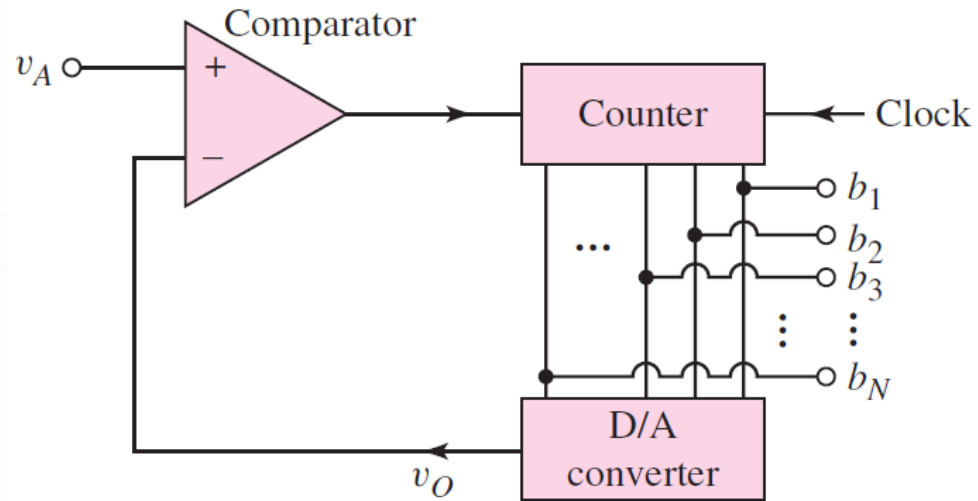
## ② Counting A/D



Initially the output of the counter is set equal to zero and the output of the D/A converter is set to  $v_O = \frac{1}{2} \text{ LSB}$ .



- When an analog input voltage  $v_A$  is applied, the output of the comparator is high (unless  $v_A < \frac{1}{2} \text{ LSB}$ ), which enables the counter.
- Then for each clock pulse, the output of the counter increases by one, producing an N-bit digital output.
- When the output of the D/A becomes just greater than the analog input voltage, the output of the comparator goes low and the counter is disabled.
- The N-bit digital output then corresponds to the analog input signal.

# Analog-to-Digital Converters

## ② Counting A/D

 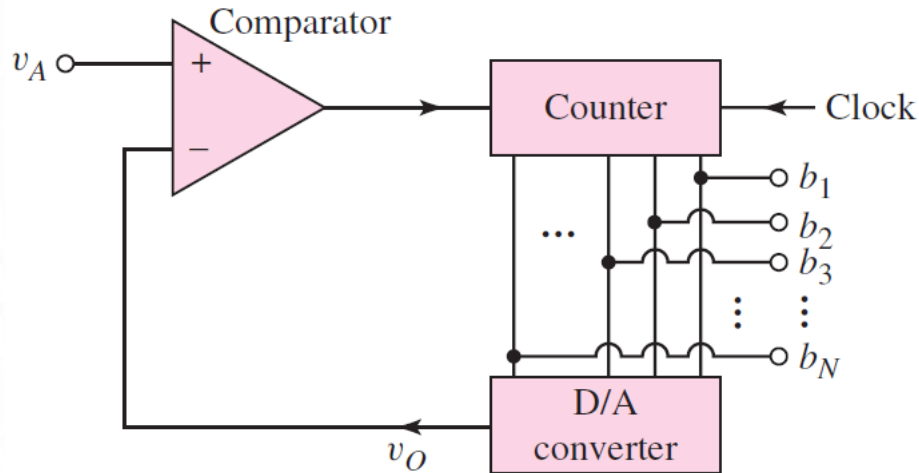

The timing diagram of a counting converter for a 4-bit digital output

- Assume that the analog input signal is in the range  $0 \leq v_A \leq 5 \text{ V}$ .
- A 1 LSB then corresponds to  $5/16 \text{ V}$ .

# Analog-to-Digital Converters

## ② Counting A/D


Assume the analog input signal is  $v_A = 5.2 \left( \frac{5}{16} \right) V$ .

The initial output of the D/A, as mentioned, is a  $1/2 \text{ LSB offset voltage}$ .

By including the offset voltage, the maximum quantization error will then be  $\pm 1/2 \text{ LSB}$ .

After the fifth clock pulse, the output of the D/A:
 
$$v_O = \frac{1}{2} \left( \frac{5}{16} \right) + 5 \left( \frac{5}{16} \right) = 5.5 \left( \frac{5}{16} \right) V$$



# Analog-to-Digital Converters

## ② Counting A/D


$$v_O = \frac{1}{2} \left( \frac{5}{16} \right) + 5 \left( \frac{5}{16} \right) = 5.5 \left( \frac{5}{16} \right) \text{ V}$$

which is larger than  $v_A$ .

✿ The counter then stops counting and the digital output is 0101.

✿ The digital output corresponds to  $5 \left( \frac{5}{16} \right) \text{ V}$ , which is within 1/2 LSB of the analog input signal.

 ✿ To complete the conversion process, the clock must go through its complete cycle, which for a 4-bit output is 16 clock periods.






# Analog-to-Digital Converters
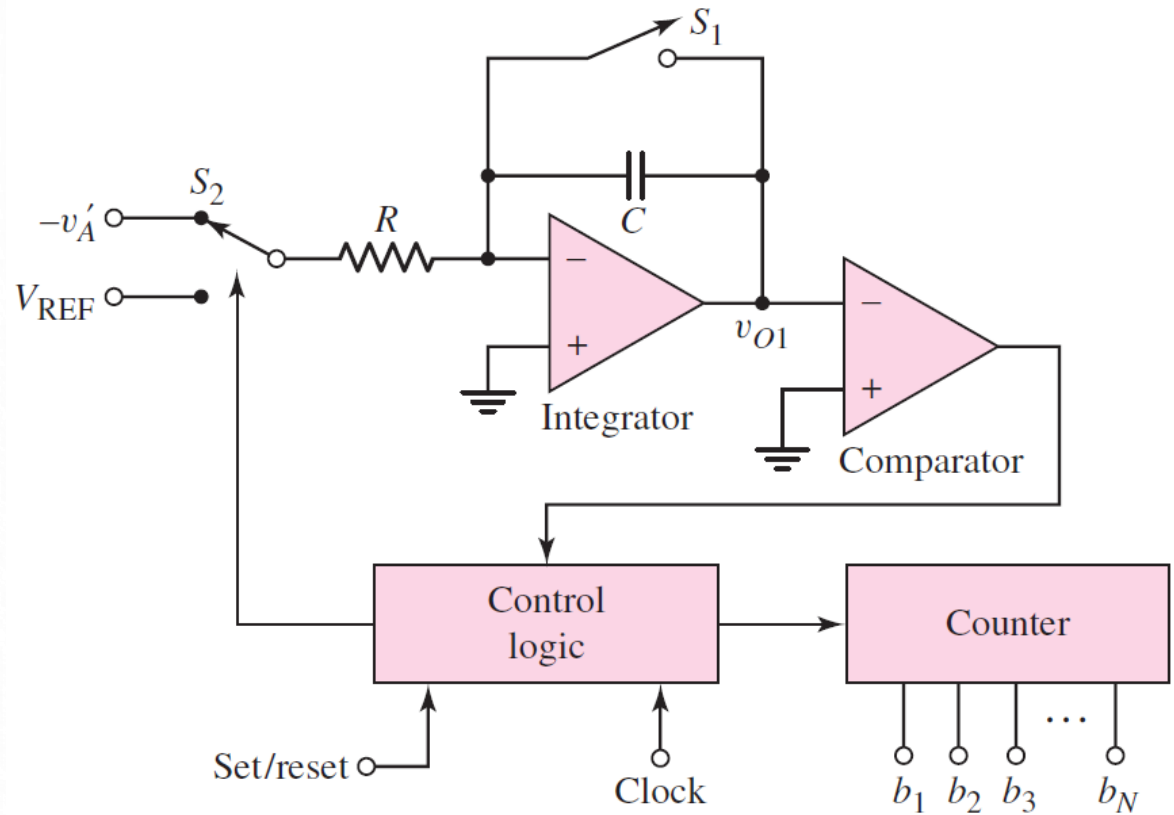
## ③ Dual-Slope A/D

✿ This type of converter is found in high-resolution data acquisition systems.

✿ At  $t = 0$ , the reset switch  $S_1$  opens and a negative input signal ( $-v'_A$ ) is applied to the integrator.





✿ The input signal  $v'_A$  is a sampled portion of the analog signal  $v_A$  and hence is a constant during the conversion process.



# Analog-to-Digital Converters



## ③ Dual-Slope A/D

 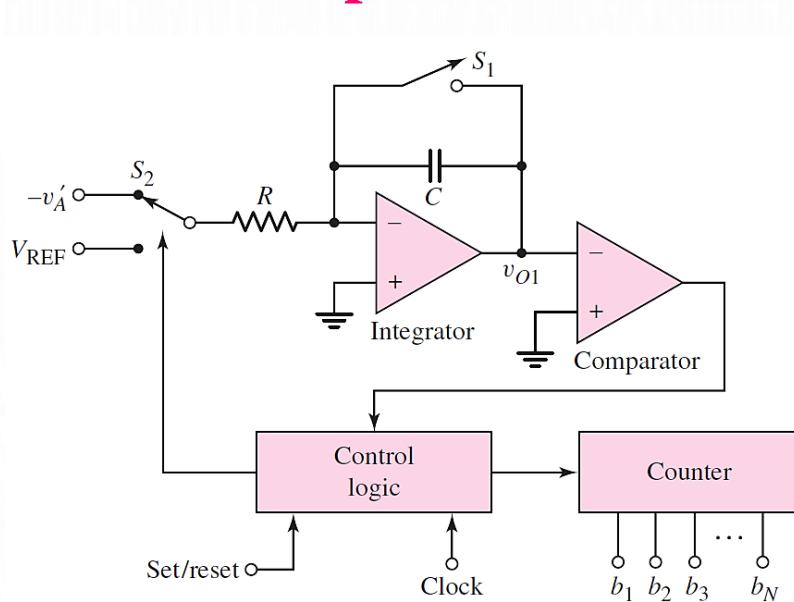

- ✿ The output  $v_{O1}$  of the integrator is a positive linear signal.
- ✿ The slope of the signal is proportional to the value of  $v'_A$ .
- ✿ This portion of the conversion process continues for a fixed time  $T_1$ , at which time the counter has reached its maximum value and overflows.
- ✿ At this time, the input switch  $S_2$  changes to a positive input reference voltage  $V_{REF}$ .

# Analog-to-Digital Converters



## ③ Dual-Slope A/D

 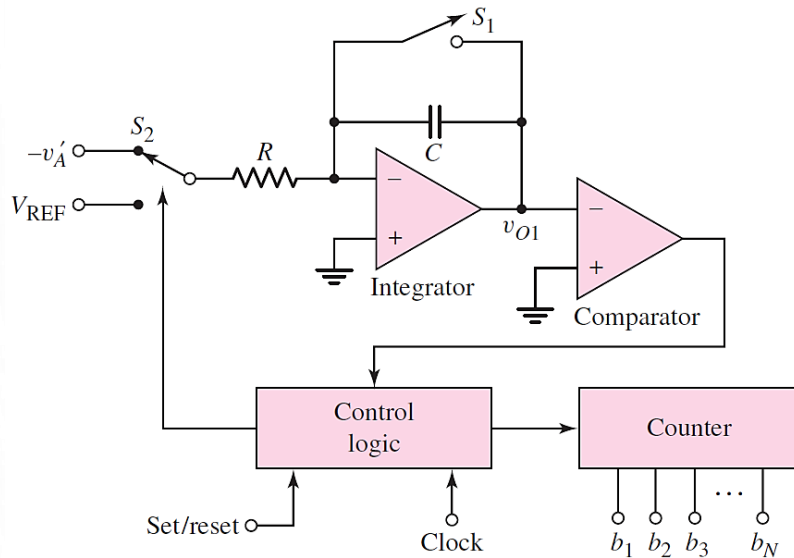

- ✿ The output of the integrator starts at the peak output voltage reached at  $T_1$  and now has a negative slope.
- ✿ The counter has been reset and is now counting.
- ✿ The counting stops when the output voltage  $v_{O1}$  reaches zero.

# Analog-to-Digital Converters

## ③ Dual-Slope A/D

  



✿ The time  $T_2$  is related to  $T_1$  and  $v'_A$  by: 
$$T_2 = T_1 \left( \frac{v'_A}{V_{REF}} \right)$$

✿ The counter reading at  $T_2$  is given by: 
$$n = 2^N \left( \frac{v'_A}{V_{REF}} \right)$$

✿ The output of the counter is then the digital equivalent of  $v'_A$ .

# Analog-to-Digital Converters



## ③ Dual-Slope A/D

  

- ✿ The output is independent of the actual values of  $R$  and  $C$  and hence is very accurate.
- ✿ The disadvantage of this data converter is that it is a fairly slow system.
- ✿ The time  $T_1$  requires  $2^N$  clock pulses and the maximum possible time  $T_2$  would also require  $2^N$  clock pulses.
- ✿ For example, a 12-bit A/D converter would require a total of 8192 clock pulses.
- ✿ This corresponds to a conversion time of 8.2 ms for a 1 MHz clock.

# Analog-to-Digital Converters

## ③ Dual-Slope A/D Conversion

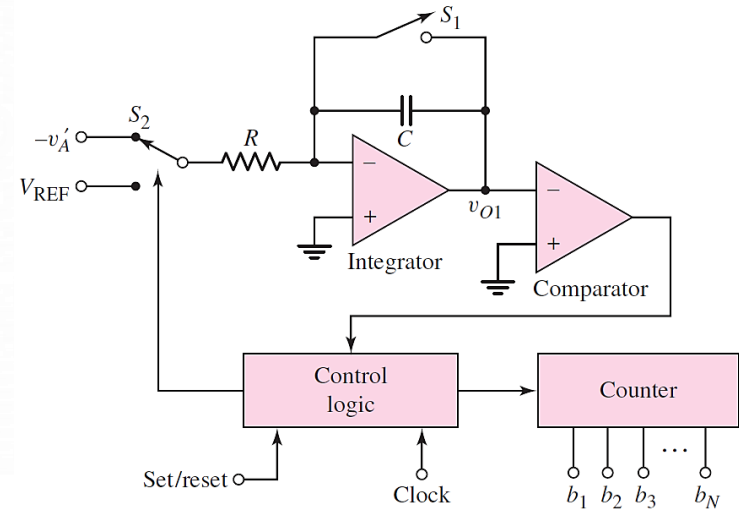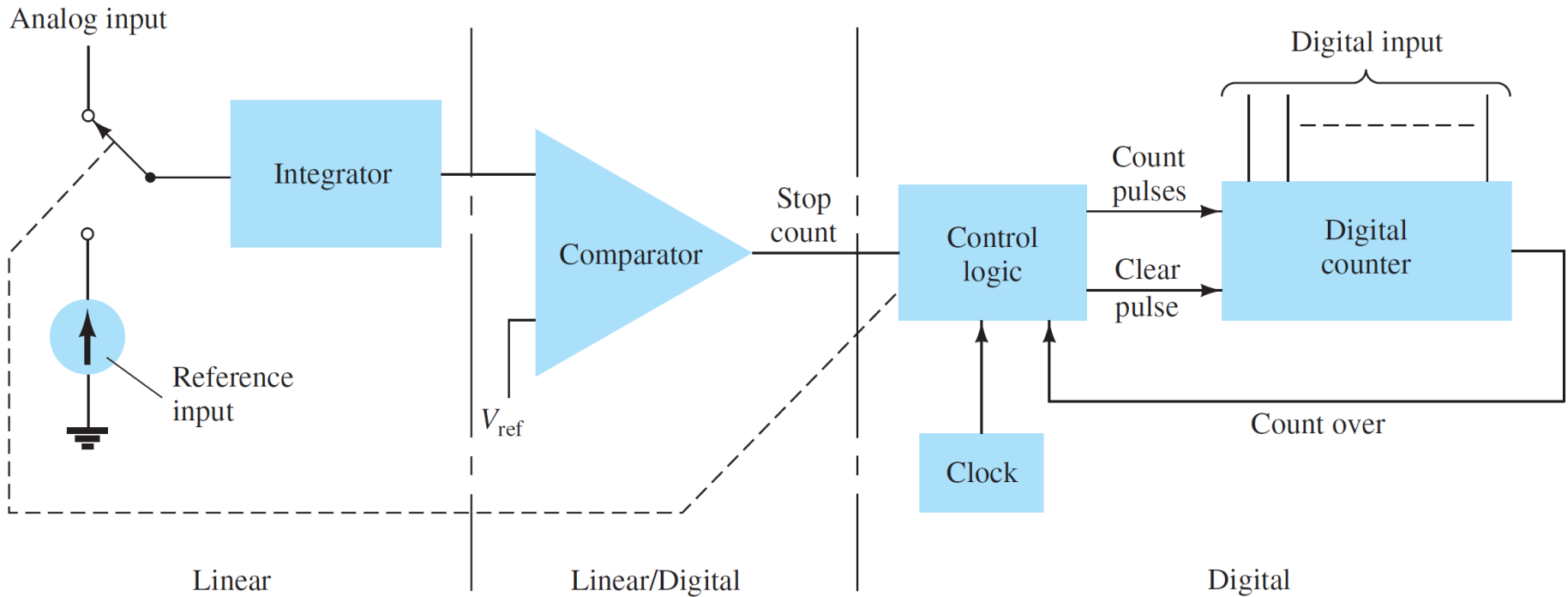

# Analog-to-Digital Converters

1. Parallel or Flash ADC
2. Counting ADC
3. Dual-Slope ADC
4. Successive Approximation A/D Converter
5. Semi-flash ADC
6. Delta-Sigma ADC
7. Pipelined ADC



# Analog-to-Digital Converters :: Comparison

ADC Type	Pros	Cons	Max Resolution	Max Sampling Rate	Main Applications	Cost	Accuracy
<b>Successive Approximation (SAR)</b>	Good speed/resolution ratio	No inherent anti-aliasing protection	8-18 bits	10 MHz (2-5 MHz Typical)	Data Acquisition	Low	Medium
<b>Delta-Sigma (<math>\Delta\Sigma</math>)</b>	High dynamic performance, Inherent anti-aliasing protection	Hysteresis on unnatural signals	8-32bits	1 MHz	Data Acquisition, Noise & Vibration, Audio	Low	Low
<b>Dual Slope</b>	Accurate, Inexpensive	Low speed	12-20 bits	100 Hz	Voltmeters	Medium	High
<b>Pipelined</b>	Very fast	Limited resolution	6-16 bits	1 GHz	Oscilloscopes	High	Low
<b>Flash</b>	Fastest	Low bit resolution	4-12 bits	10 GHz	Oscilloscopes	High	Low




# Analog-to-Digital Converters

## ④ Successive Approximation A/D Converter (SAR)

✿ The basic elements in the architecture




Analog Input

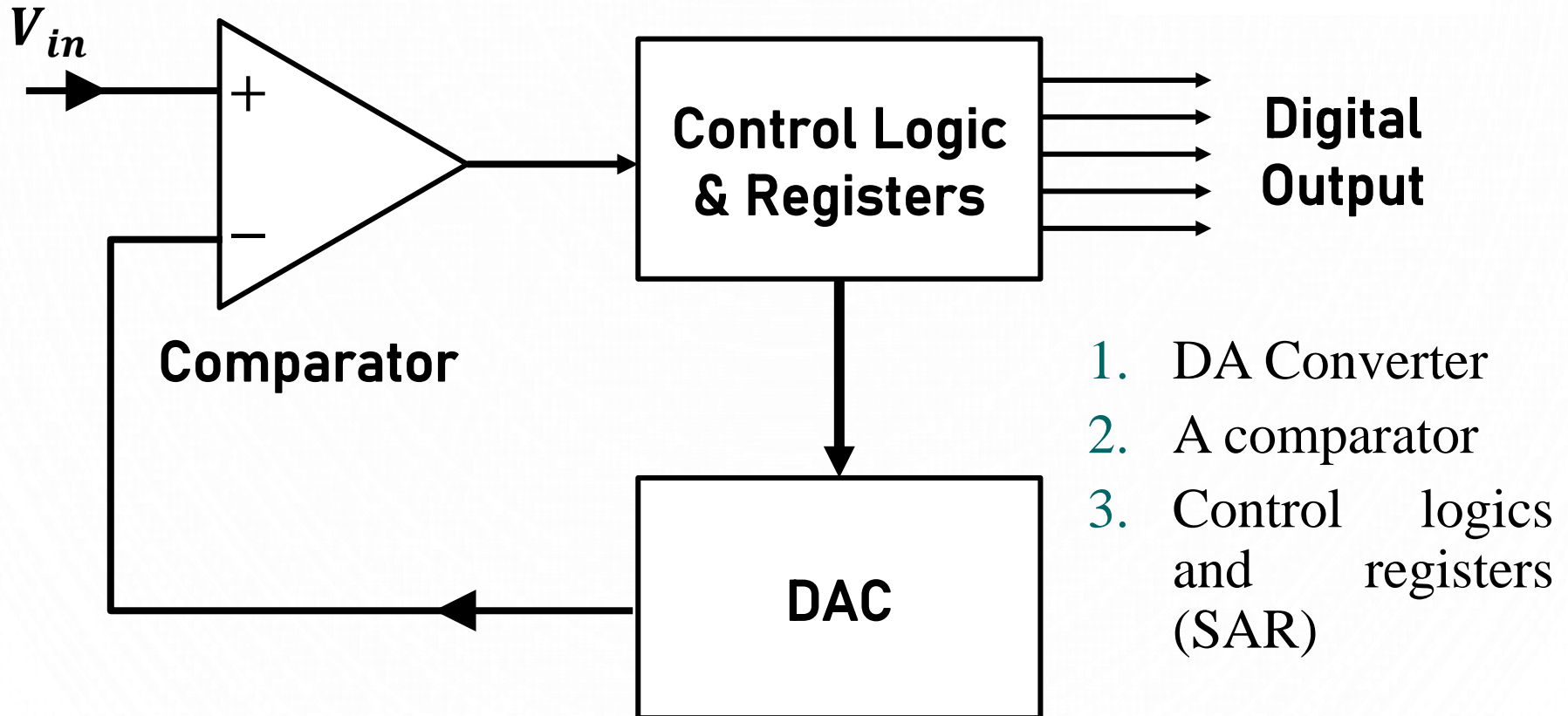

# Analog-to-Digital Converters
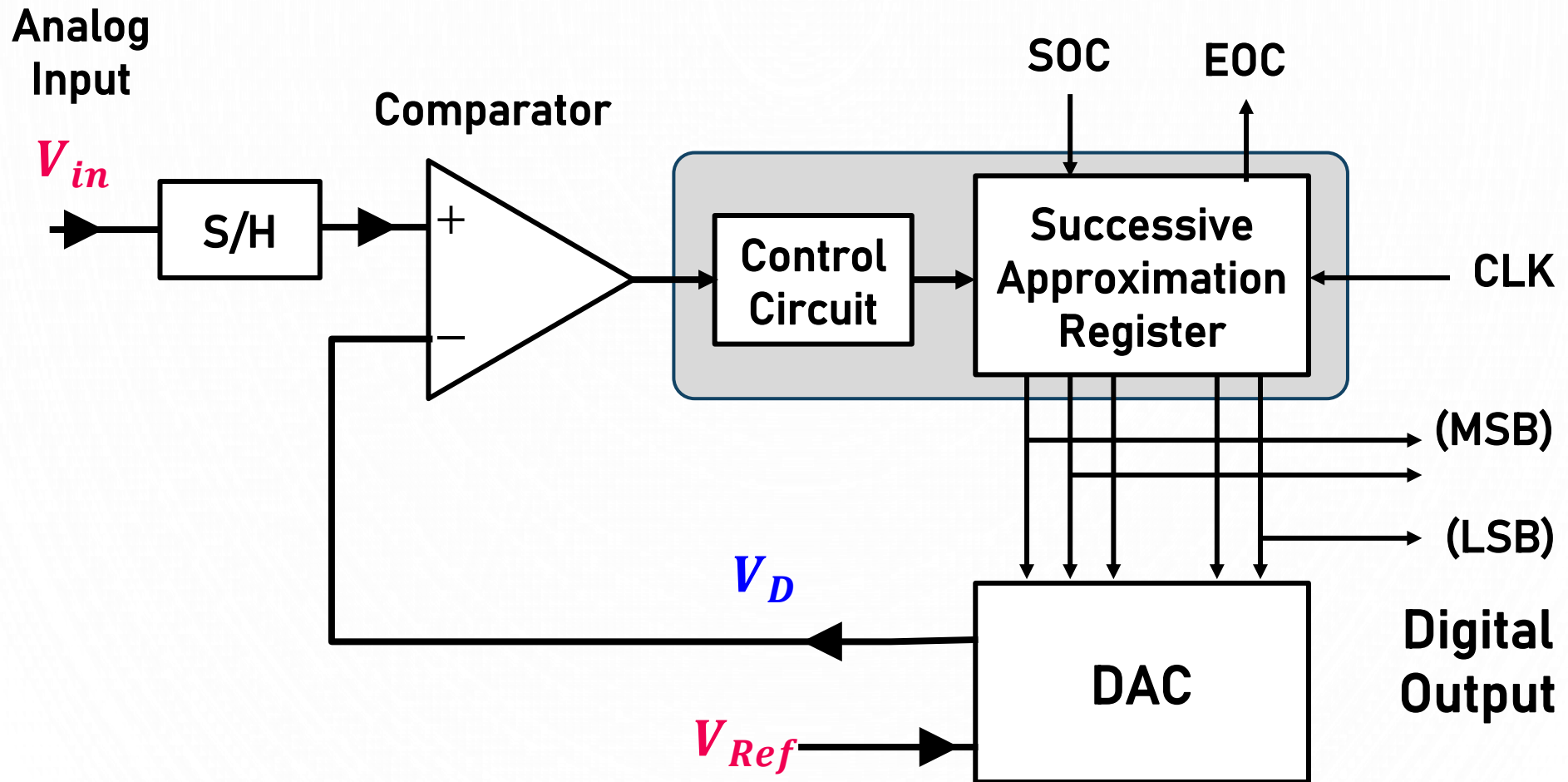
## ④ Successive Approximation A/D Converter (SAR)




Start of Conversion indicator (SOC), End of Conversion indicator (EOC)

# Analog-to-Digital Converters

## ④ Successive Approximation A/D Converter (SAR)


### 4-bit conversion

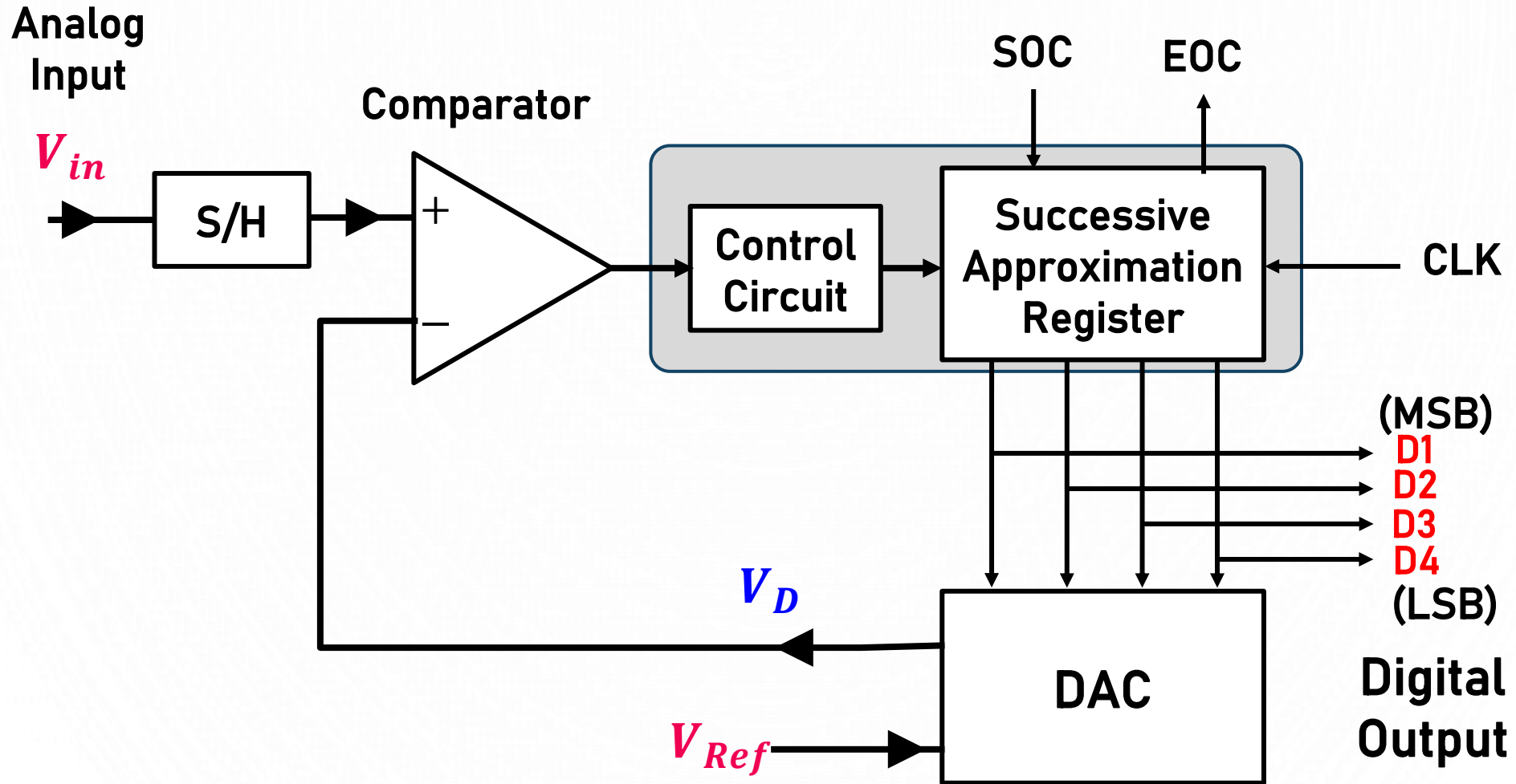

## Ex. Successive Approximation A/D Converter (SAR)

Convert an analog signal  $V_{in} = 11.2 \text{ V}$  to digital using 4-bit ADC. The reference voltage of DAC is  $V_{Ref} = 16 \text{ V}$ .

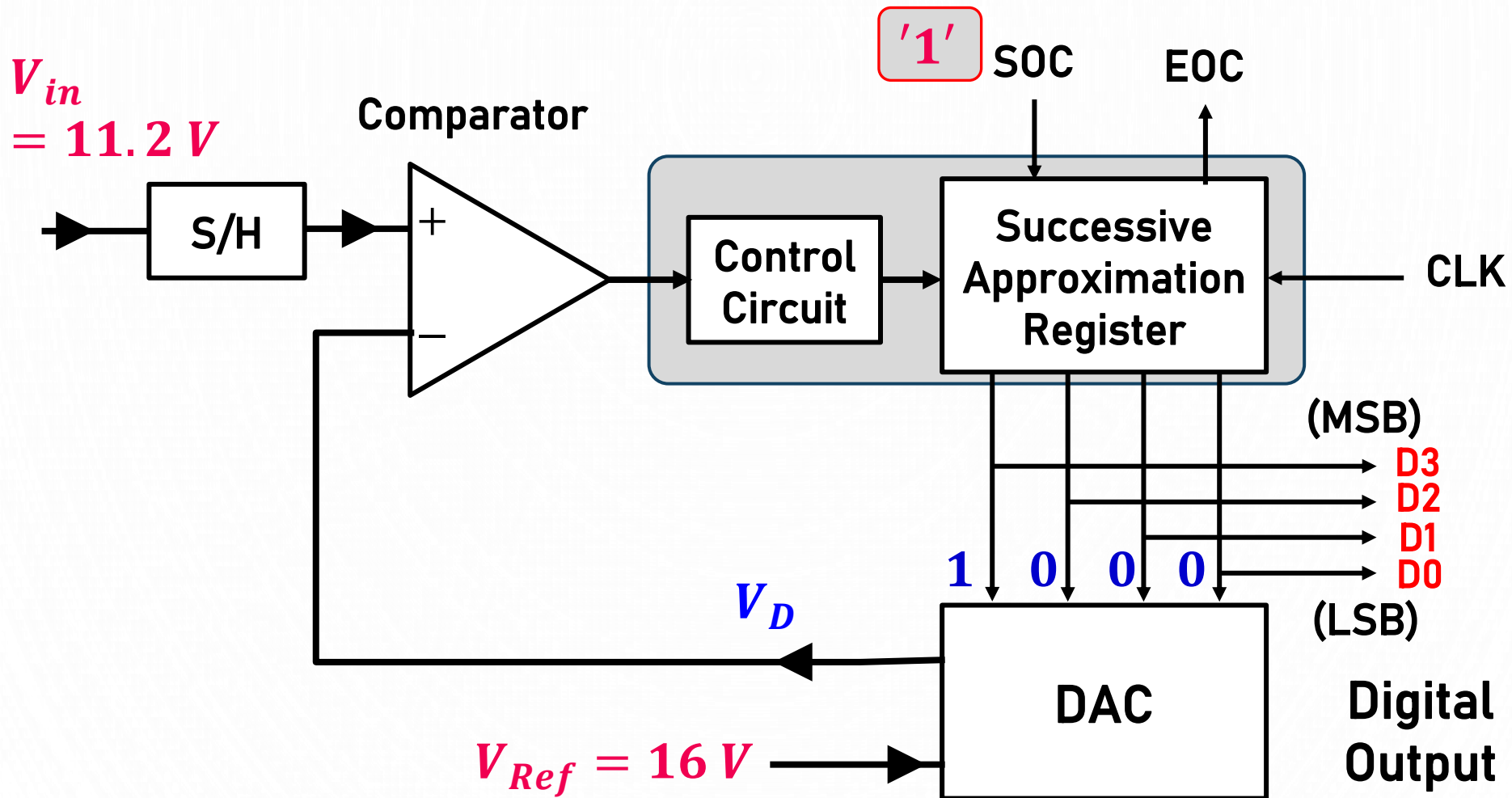
# Ex. Successive Approximation A/D Converter (SAR)




$$1000 \rightarrow V_{Ref} \left( \frac{D3}{2} + \frac{D2}{4} + \frac{D1}{8} + \frac{D0}{16} \right) = 8 V = \frac{V_{ref}}{2}$$
 
# Ex. Successive Approximation A/D Converter (SAR)

$V_{in} = 11.2\text{ V}$     4-bit ADC     $V_{Ref} = 16\text{ V}$


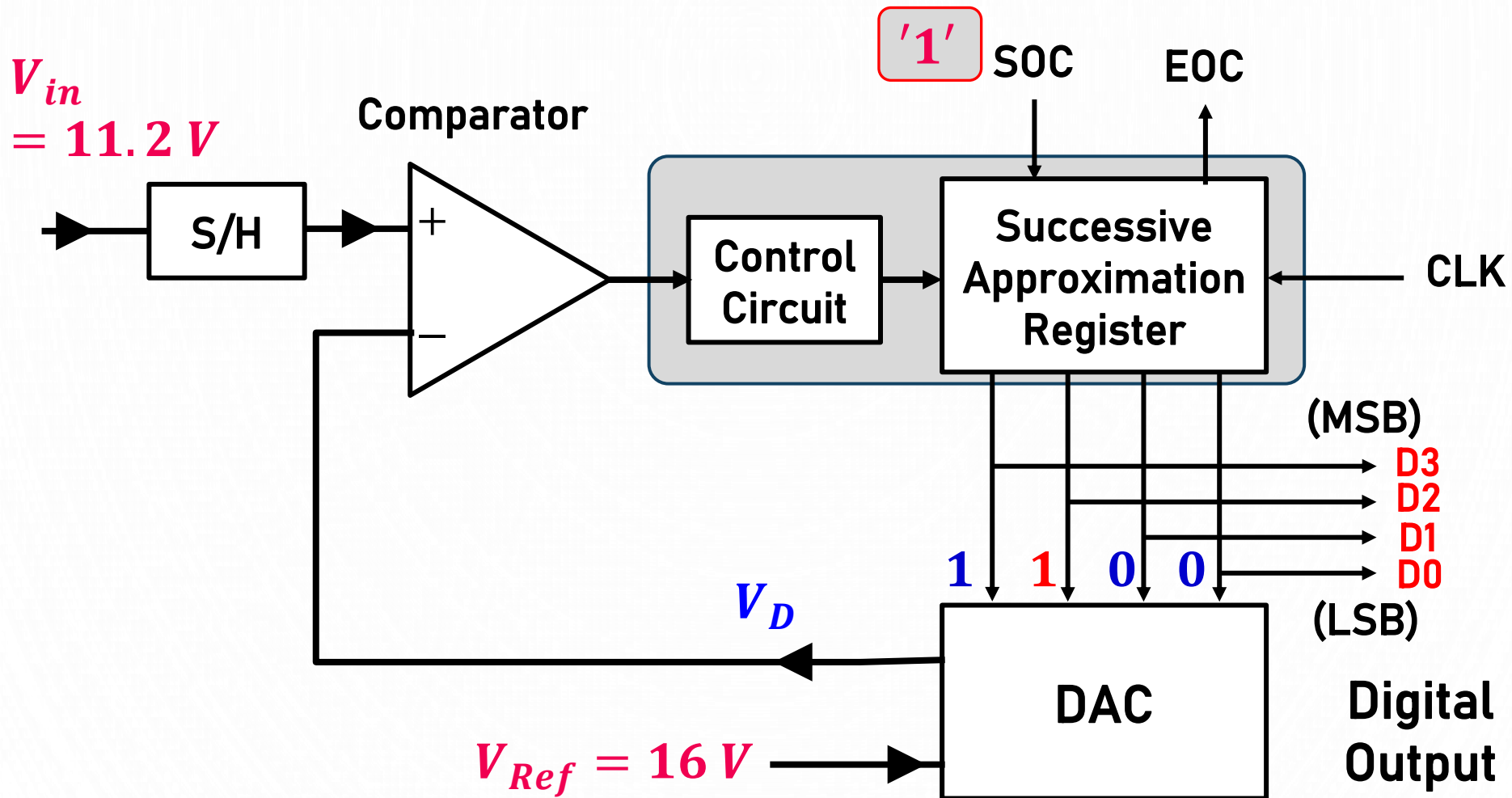
# Ex. Successive Approximation A/D Converter (SAR)




$$1 \ 1 \ 0 \ 0 \Rightarrow V_{Ref} \left( \frac{D3}{2} + \frac{D2}{4} + \frac{D1}{8} + \frac{D0}{16} \right) = 12 V$$



 
# Ex. Successive Approximation A/D Converter (SAR)

$V_{in} = 11.2 V$     4-bit ADC     $V_{Ref} = 16 V$



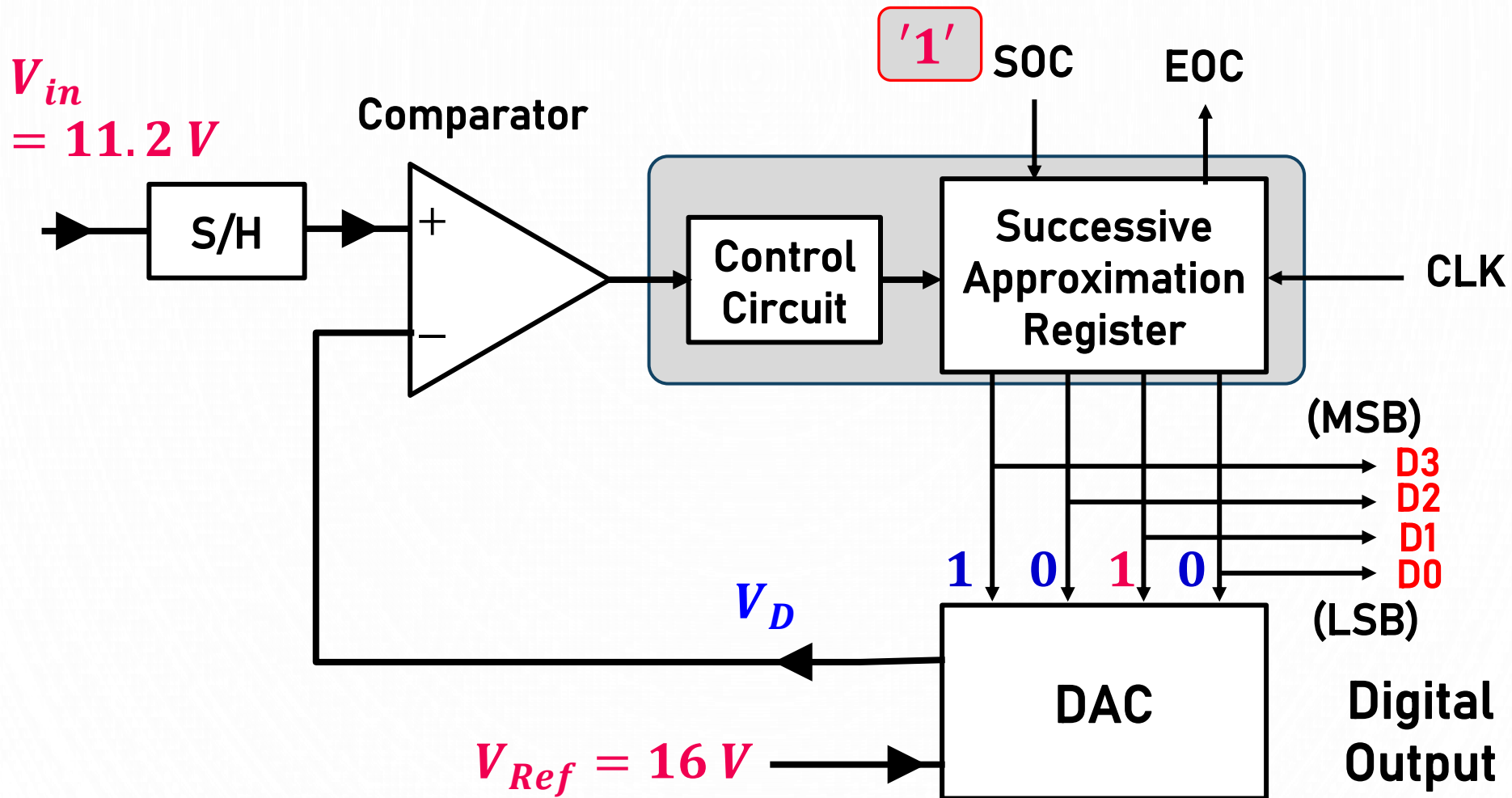
# Ex. Successive Approximation A/D Converter (SAR)



$$1\ 0\ 1\ 0 \Rightarrow V_{Ref} \left( \frac{D3}{2} + \frac{D2}{4} + \frac{D1}{8} + \frac{D0}{16} \right) = 10\text{ V}$$
 
# Ex. Successive Approximation A/D Converter (SAR)

$V_{in} = 11.2\text{ V}$     4-bit ADC     $V_{Ref} = 16\text{ V}$



# Analog-to-Digital Converters

## ④ Successive Approximation A/D Converter (SAR)

✿ Conversion time Independent of the input voltage

$$T_C = N \times T_{CLK}$$