

---

**EE 254**

# **Electronic Instrumentation**

**Dr. Tharindu Weerakoon**

Dept. of Electrical and Electronic Engineering

*Faculty of Engineering, University of Peradeniya*


---

***Week #03 – Lecture Note #07***

# Low-Pass and High-Pass Filters - More Examples -

## Ex. 05

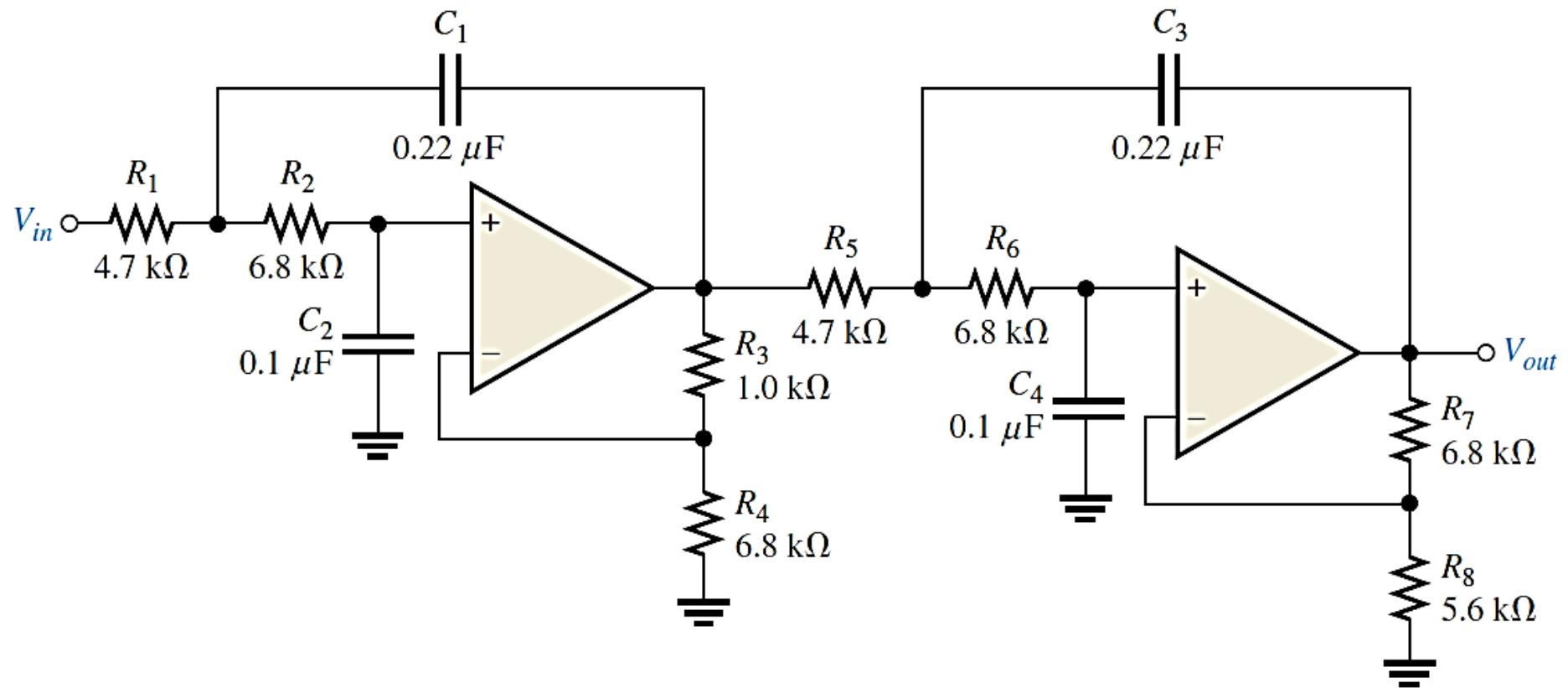- a) Is the four-pole filter in Figure below approximately optimized for a Butterworth response? What is the roll-off rate?



## Ex. 05 (cont'd)

### High Pass

First Stage:

$$DF = 2 - \frac{R_3}{R_4} = 2 - \frac{1.0}{6.8} = 1.85$$

Second Stage:

$$DF = 2 - \frac{R_7}{R_8} = 2 - \frac{6.8}{5.6} = 0.786$$

ORDER	ROLL-OFF DB/DECADE	1ST STAGE			2ND STAGE			3RD STAGE		
		POLES	DF	$R_1/R_2$	POLES	DF	$R_3/R_4$	POLES	DF	$R_5/R_6$
1	-20	1	Optional							
2	-40	2	1.414	0.586						
3	-60	2	1.00	1	1	1.00	1			
4	-80	2	1.848	0.152	2	0.765	1.235			
5	-100	2	1.00	1	2	1.618	0.382	1	0.618	1.382
6	-120	2	1.932	0.068	2	1.414	0.586	2	0.518	1.482

## Ex. 05 (cont'd)

ORDER	ROLL-OFF DB/DECADE	1ST STAGE			2ND STAGE			3RD STAGE		
		POLES	DF	$R_1/R_2$	POLES	DF	$R_3/R_4$	POLES	DF	$R_5/R_6$
1	-20	1	Optional							
2	-40	2	1.414	0.586						
3	-60	2	1.00	1	1	1.00	1			
4	-80	2	1.848	0.152	2	0.765	1.235			
5	-100	2	1.00	1	2	1.618	0.382	1	0.618	1.382
6	-120	2	1.932	0.068	2	1.414	0.586	2	0.518	1.482

*From the table*


1<sup>st</sup> stage  $DF = 1.848$       and      2<sup>nd</sup> stage  $DF = 0.765$

Therefore, this filter is **approximately Butterworth.**

Roll-off rate = **80 dB/decade**

## Ex. 05 (cont'd)

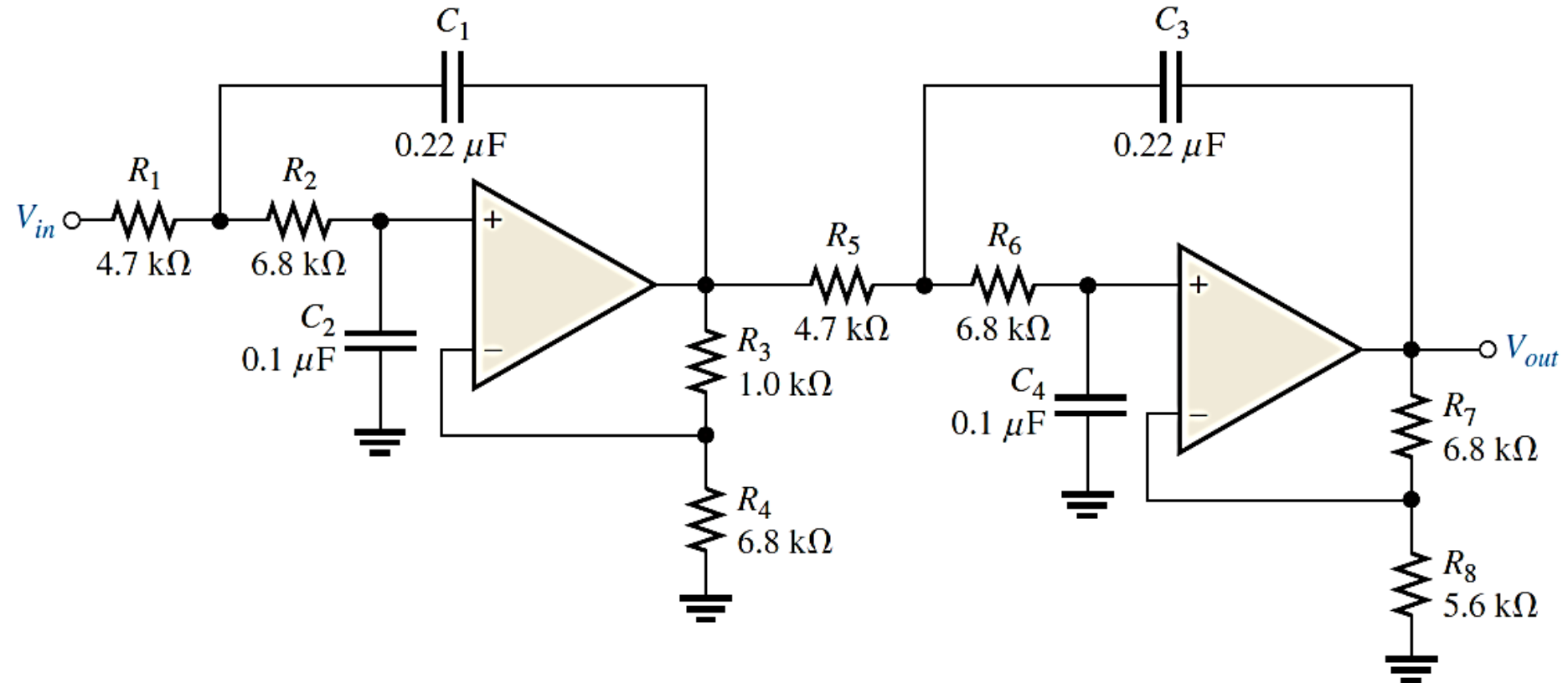
b) Determine the critical frequency of the filter circuit below.



$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{2\pi\sqrt{R_5 R_6 C_3 C_4}} = \frac{1}{2\pi\sqrt{(4.7 \text{ k}\Omega)(6.8 \text{ k}\Omega)(0.22 \text{ }\mu\text{F})(0.1 \text{ }\mu\text{F})}} = \mathbf{190 \text{ Hz}}$$

## Ex. 05 (cont'd)

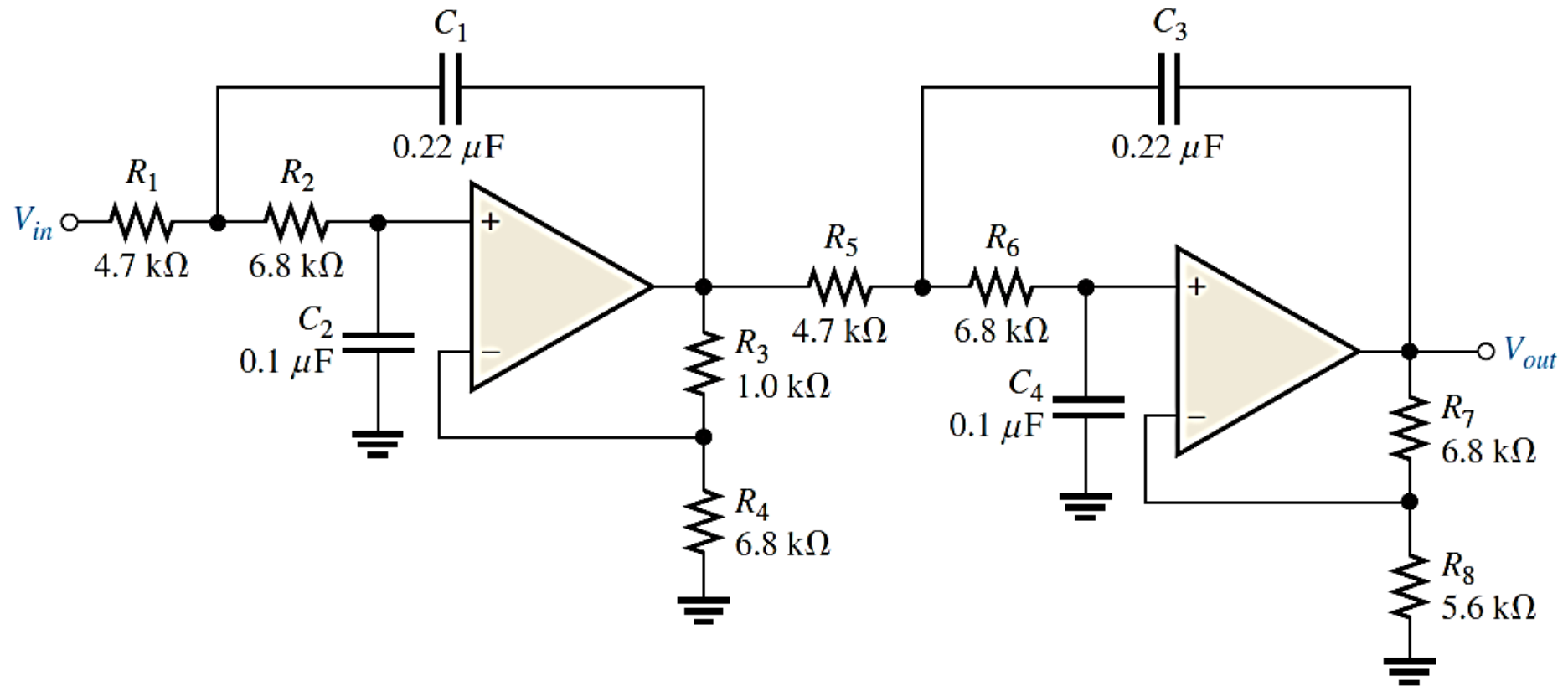- c) Without changing the response curve, adjust the component values in the filter circuit to make it an equal-value filter. Select for both stages.



## Ex. 05 (cont'd)

$$R = R_1 = R_2 = R_5 = R_6 \text{ and } C = C_1 = C_2 = C_3 = C_4$$

Let  $C = 0.22\mu F$  (for both stages)

$$f_c = \frac{1}{2\pi\sqrt{R^2C^2}} = \frac{1}{2\pi RC}$$


$$R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi(190 \text{ Hz})(0.22 \mu F)} = 3.81 \text{ k}\Omega$$

Choose  $R = 3.9 \text{ k}\Omega$  (for both stages)




## Ex. 05 (cont'd)

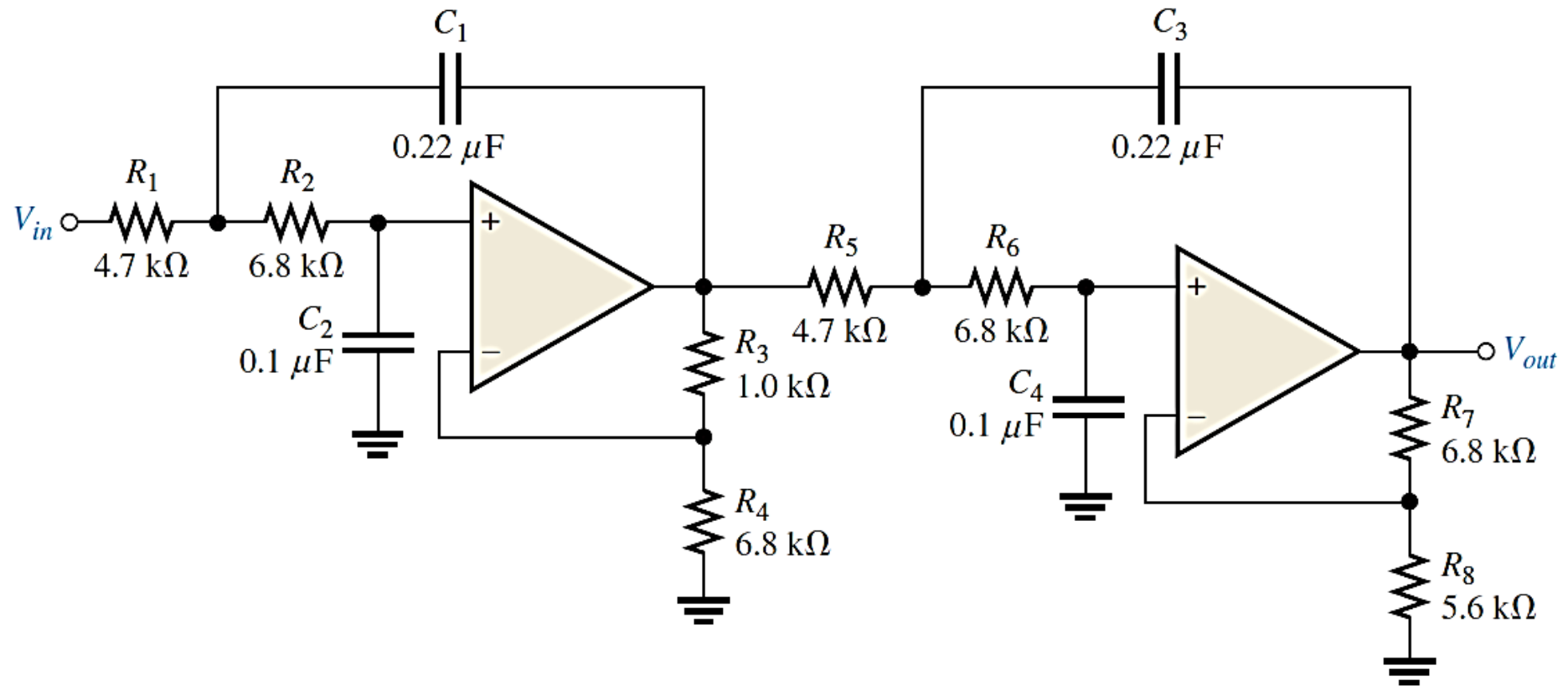- d) Modify the filter circuit in the Figure to increase the roll-off rate to  $-120$  dB/decade while maintaining an approximate Butterworth response.



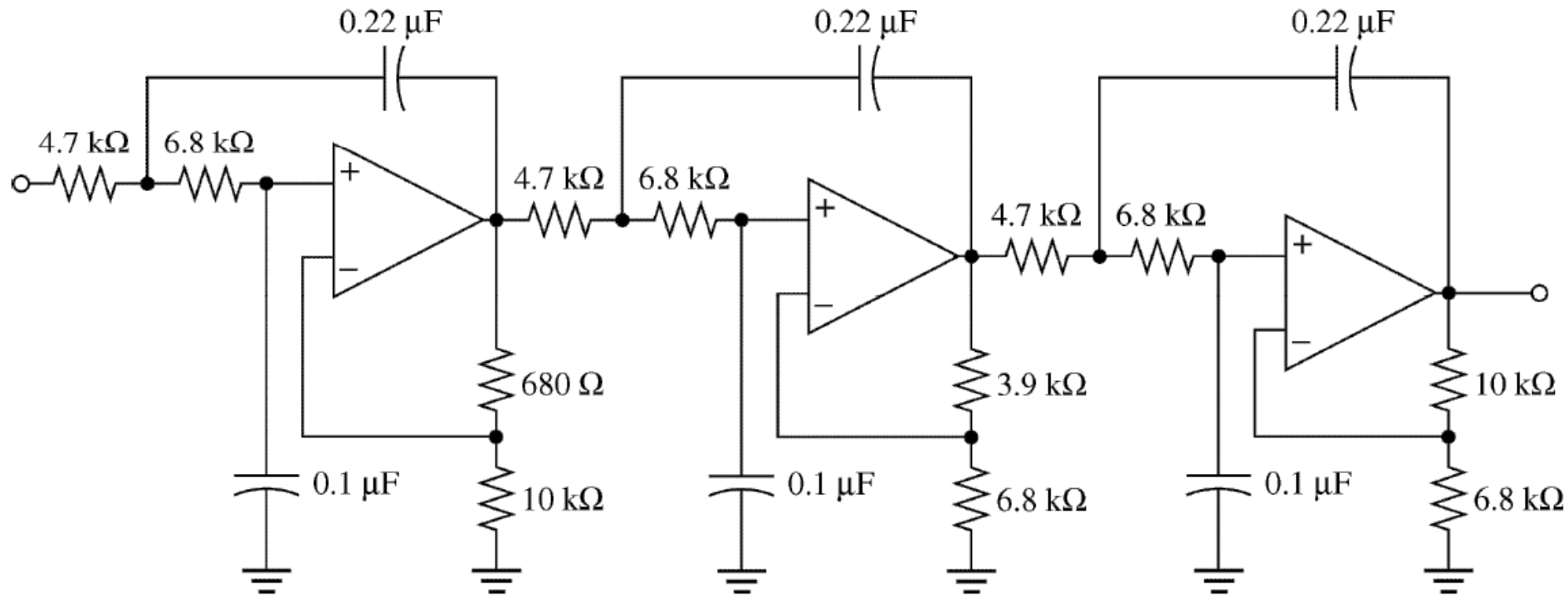
## Ex. 05 (cont'd)

Add another identical stage and change the ratio of the feedback resistors to 0.068 for first stage, 0.586 for second stage, and 1.482 for third stage.




## Ex. 06

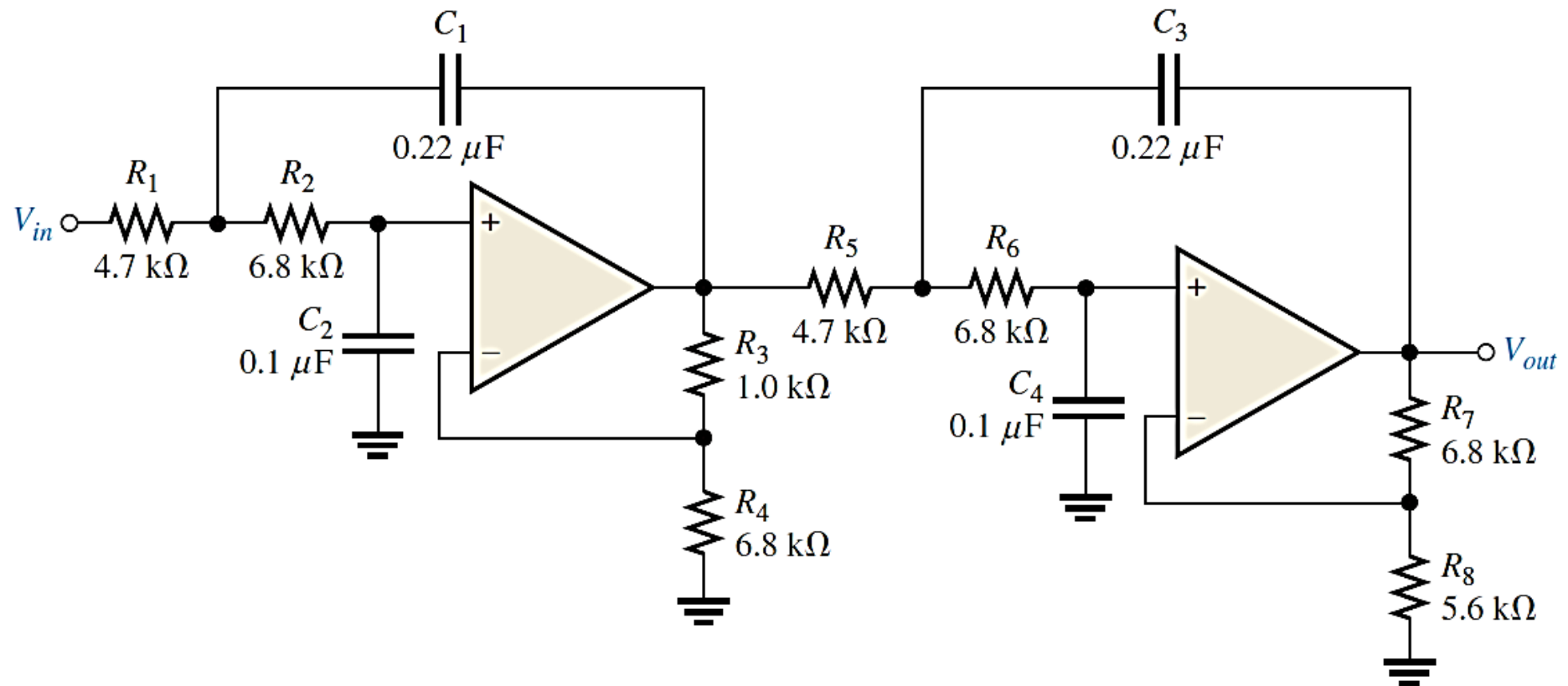- a) Convert the filter below to a high-pass with the same critical frequency and response characteristic.




## Ex. 06 (cont'd)

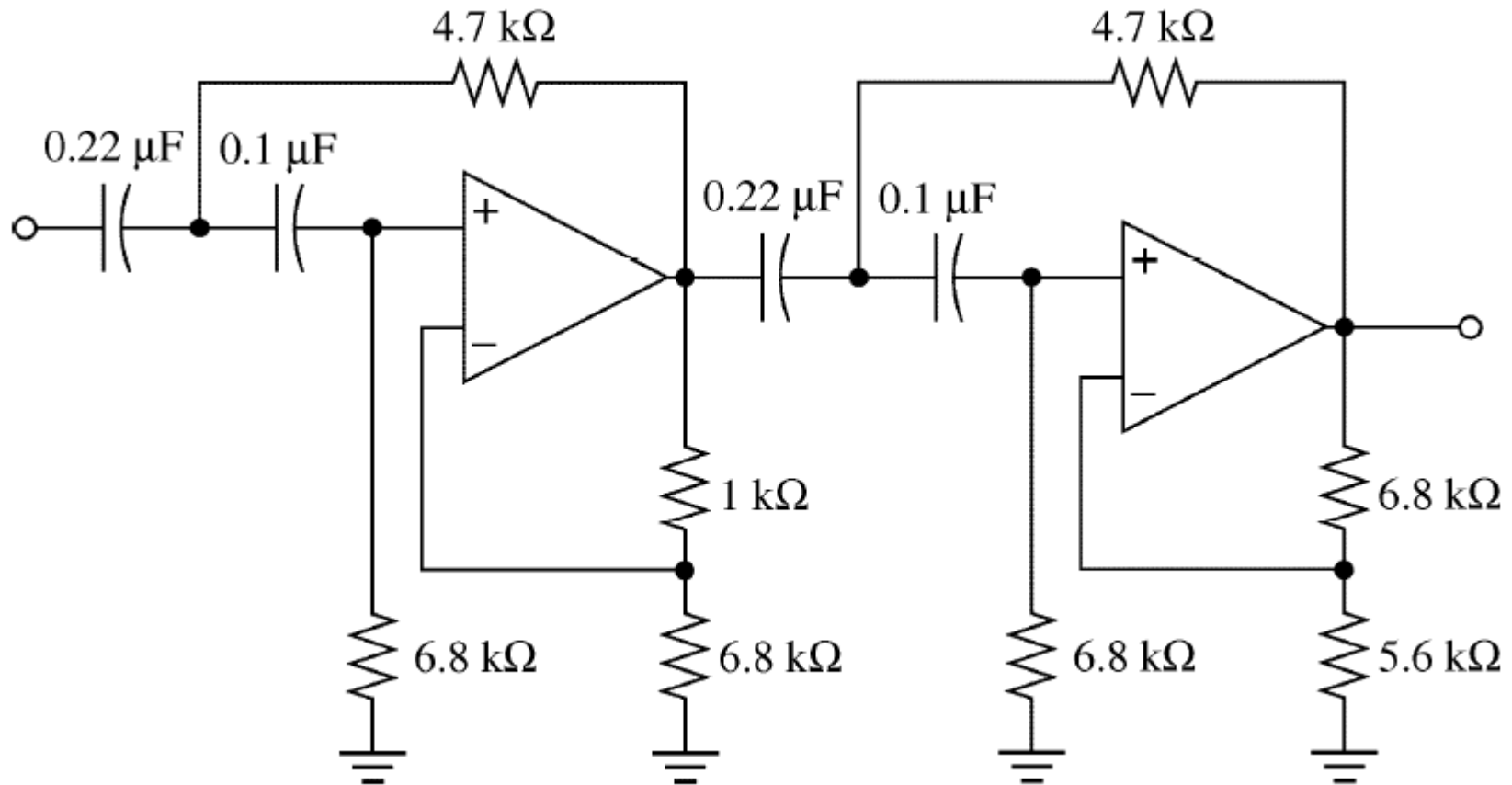

## Ex. 06 (cont'd)

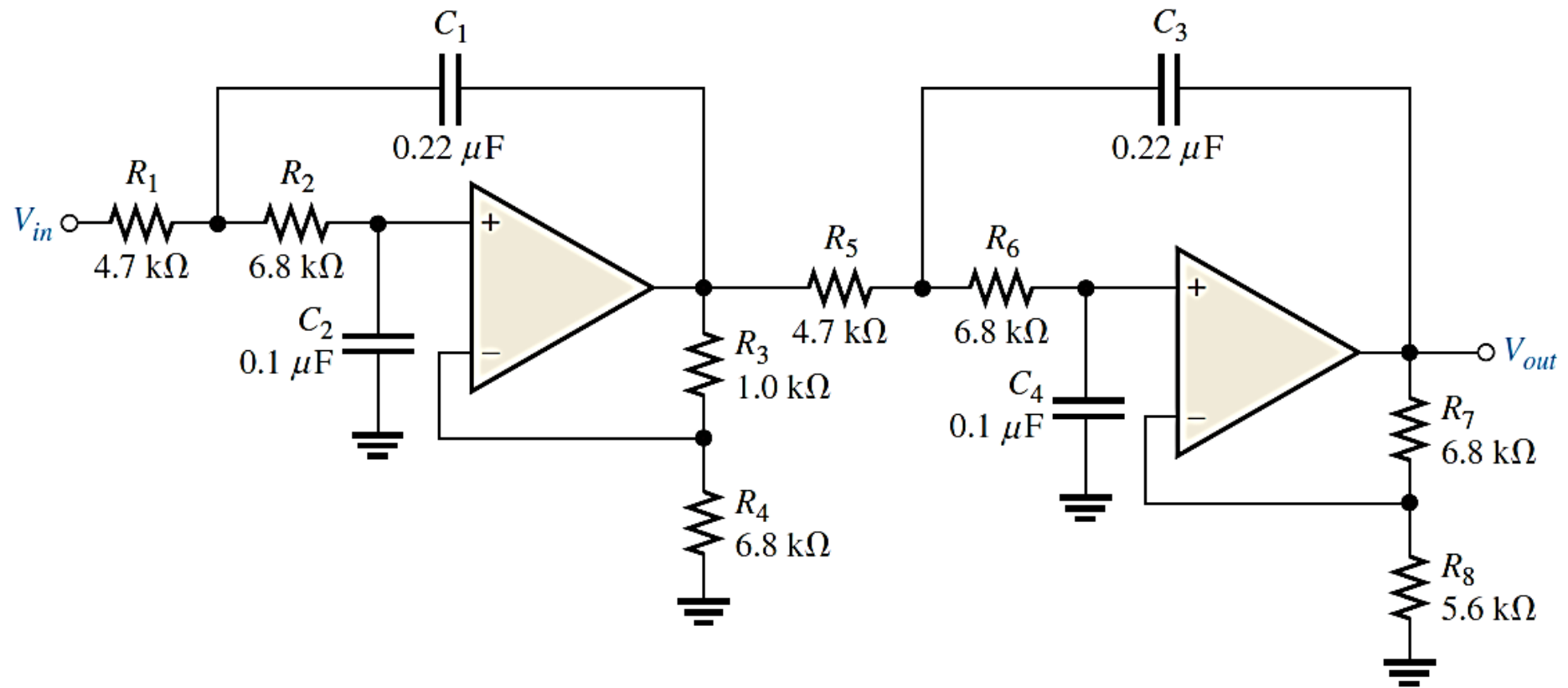- b) Make the necessary circuit modification to reduce by half the critical frequency in Ex. 05(b).



## Ex. 06 (cont'd)

$$f_c = \frac{1}{2\pi RC}$$

$$f_0 = \frac{190 \text{ Hz}}{2} = 95 \text{ Hz}$$


$$R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi(95 \text{ Hz})(0.22 \mu\text{F})} = 7615 \Omega$$

Let  **$R = 7.5 \text{ k}\Omega$** .


And choose  $R_1, R_2, R_3$  and  $R_6$  to  **$7.5 \text{ k}\Omega$**

## Ex. 06 (cont'd)

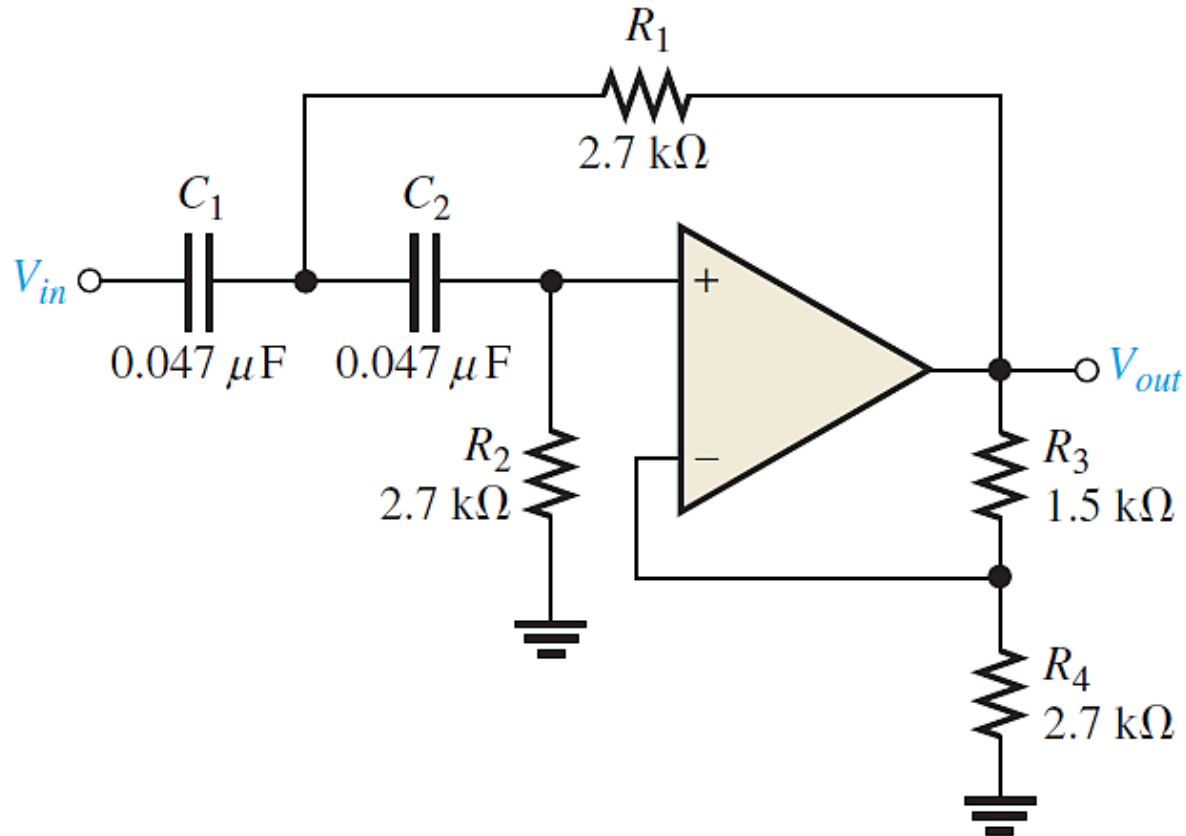- c) For the filter in Figure below,
- how would you increase the critical frequency?
  - How would you increase the gain?



## Ex. 06 (cont'd)

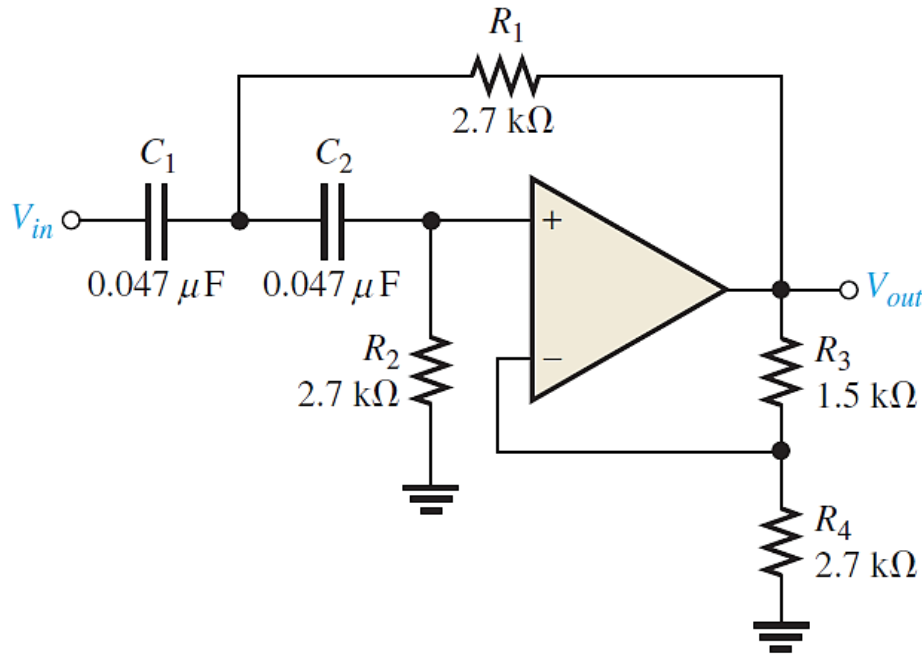

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}}$$

$$A_{cl(NI)} = \frac{R_3}{R_4} + 1$$

- i. Decrease  $R_1$  and  $R_2$  or  $C_1$  and  $C_2$ .
- ii. Increase  $R_3$  or decrease  $R_4$ .