
EE 254

Electronic Instrumentation

Dr. Tharindu Weerakoon

Dept. of Electrical and Electronic Engineering

Faculty of Engineering, University of Peradeniya

Lecture Note #10

Content (Brief)

2. Op-Amp Applications

* Linear Applications

- ❖ Inverting amplifiers
- ❖ Noninverting amplifiers
- ❖ Differential amplifiers
- ❖ Summing amplifiers
- ❖ Integrators
- ❖ Differentiators
- ❖ Low/ High pass filters
- ❖ Instrumentational amplifiers

* Nonlinear Applications

- ❖ Precision rectifiers
- ❖ Peak detectors
- ❖ Schmitt-trigger comparator
- ❖ Logarithmic amplifiers



- ① Precision Rectifiers
- ② Peak Detectors
- ③ Logarithmic Amplifiers

① Precision Half-Wave Rectifier

☼ For $v_I \geq 0$



$$v_O = v_I$$

Super-diode

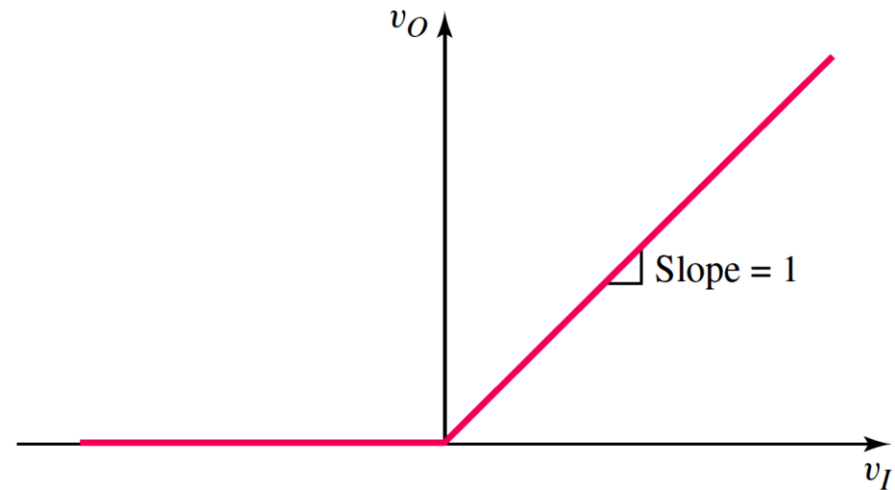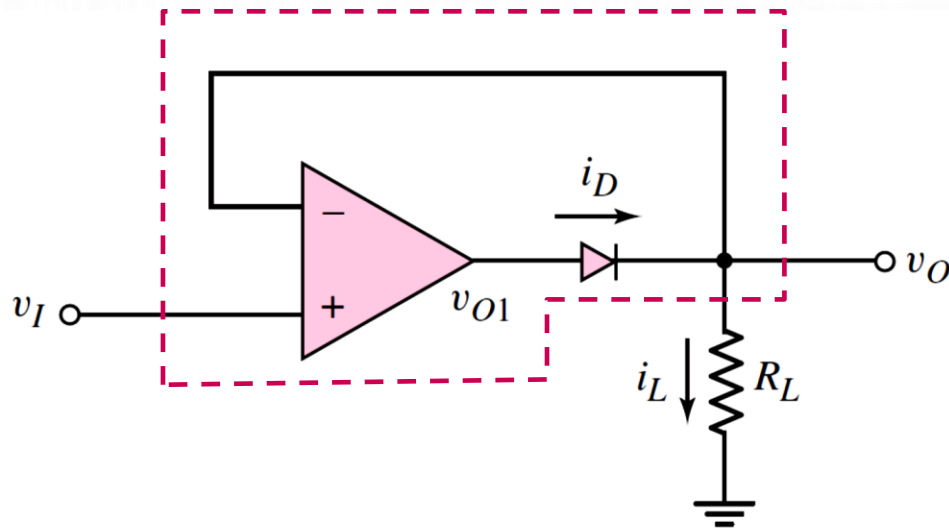


① Precision Half-Wave Rectifier

Simple half-wave rectifier circuit

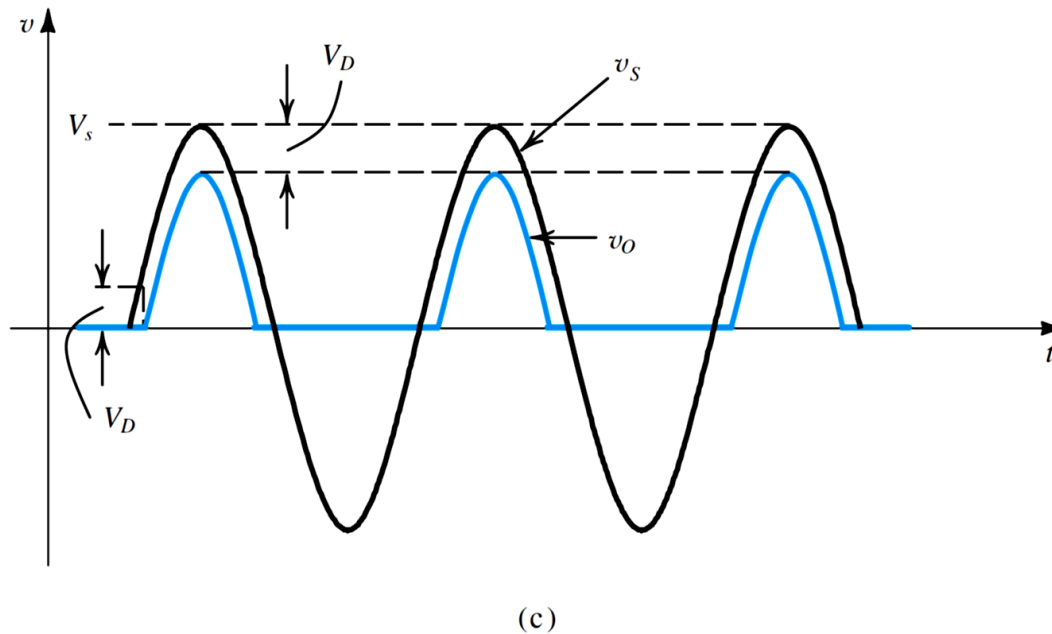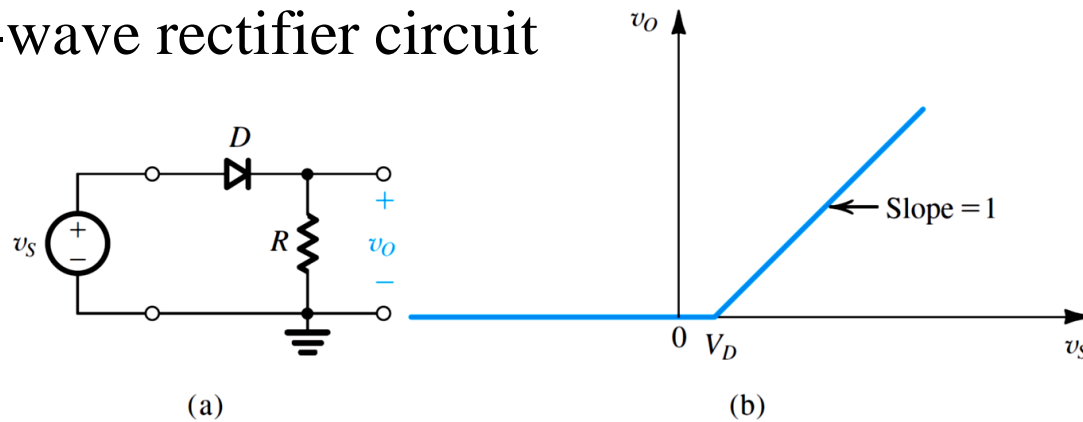

② Peak Detector

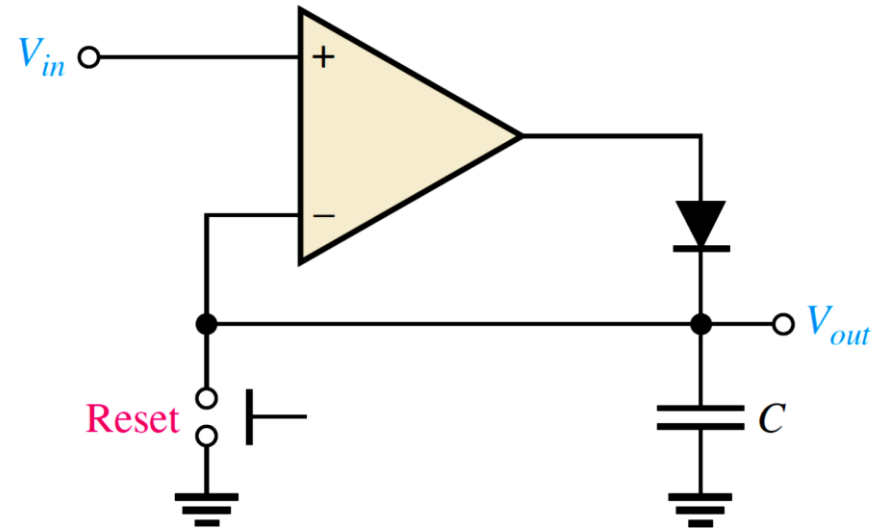- ❁ An interesting application of the op-amp is in a peak detector circuit.
- ❁ This circuit is used to detect the peak of the input voltage and store that peak voltage on a capacitor.
- ❁ For example, to detect and store the maximum value of a voltage surge



③ Logarithmic Amplifier

✿ The diode is to be forward biased, so the input signal voltage is limited to positive values.

✿ The diode current


$$i_D = I_S(e^{v_D/V_T} - 1)$$

✿ If the diode is sufficiently forward biased, the (-1) term is negligible

$$i_D \cong I_S e^{v_D/V_T}$$

✿ The input current

$$i_1 = \frac{v_I}{R_1}$$

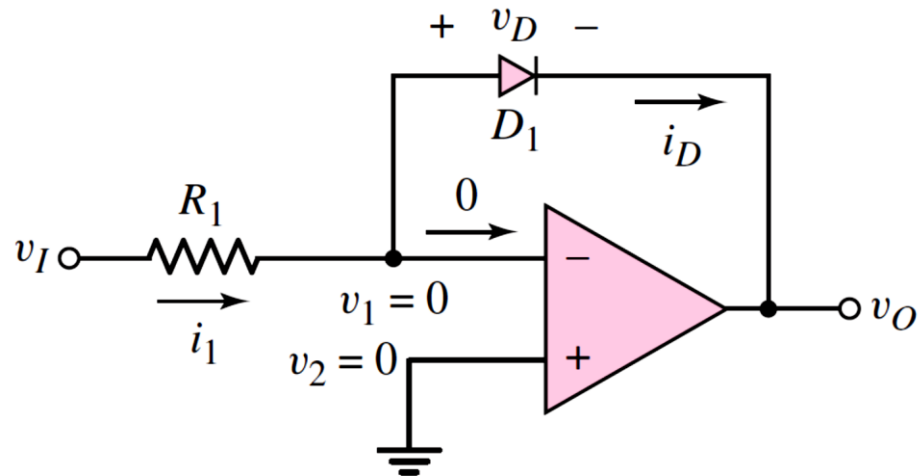

③ Logarithmic Amplifier

- The output voltage, since v_1 is at virtual ground

$$v_O = -v_D$$


- Noting that $i_1 = i_D$,

$$i_1 = \frac{v_I}{R_1} = i_D = I_S e^{-v_O/V_T}$$

- Take the natural log of both sides

$$\ln \left(\frac{v_I}{I_S R_1} \right) = -\frac{v_O}{V_T}$$

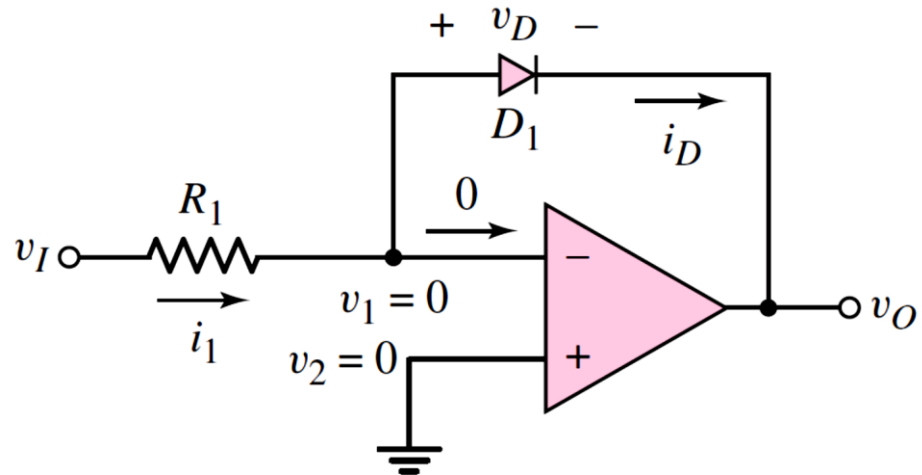
$$v_O = -V_T \ln \left(\frac{v_I}{I_S R_1} \right)$$



③ Logarithmic Amplifier

$$v_O = -V_T \ln \left(\frac{v_I}{I_S R_1} \right)$$

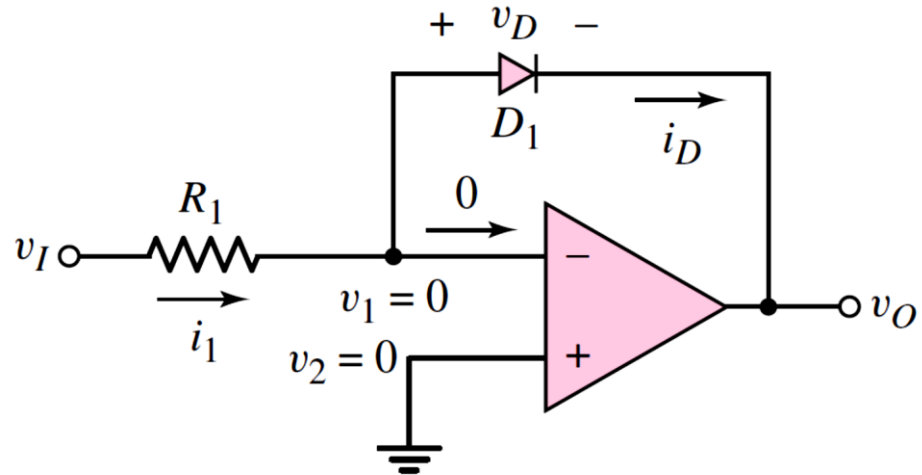
✿ The output voltage is proportional to the log of the input voltage.



✿ Analyze the disadvantages of this circuit configuration and explain the solutions to overcome them.

④ Antilog or Exponential Amplifier

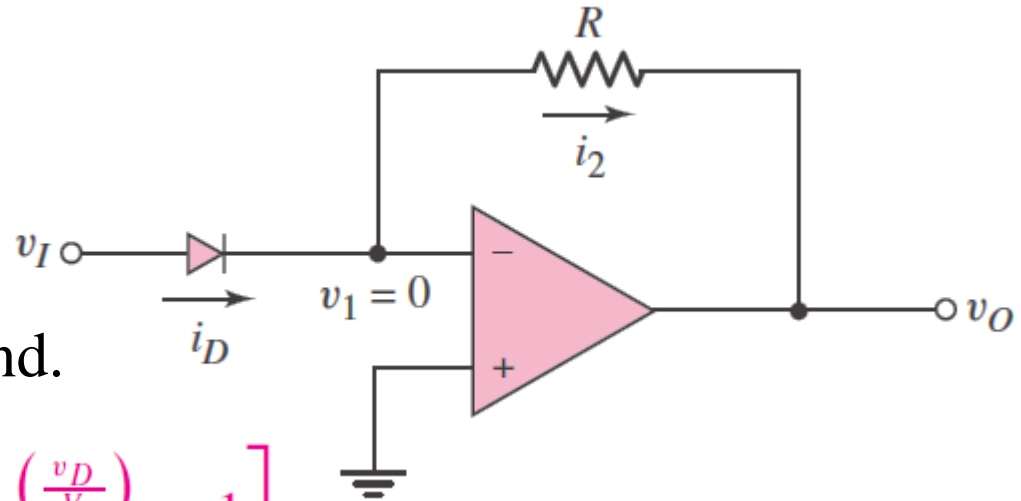- Example using a diode as the current through the diode is in exponential form.
 $v_I > 0$ and v_1 is virtually ground.



$$i_D \cong I_S e^{v_I/V_T} \quad i_D = I_S \left[e^{\left(\frac{v_D}{nV_T}\right)} - 1 \right]$$

and $v_O = -i_2 R = -i_D R$ or $v_O = -I_S R \cdot e^{v_I/V_T}$

- The output voltage is an exponential function of the input voltage.


v_T is the Thermal voltage approximately 0.026 V at room temperature. The parameter I_S is the **reverse-bias saturation current**. For silicon pn junctions, typical values are in the range of 10^{-18} to 10^{-12} A .

Design Examples

Summing Op-Amp Circuit Design

How to design a circuit such that the output is:
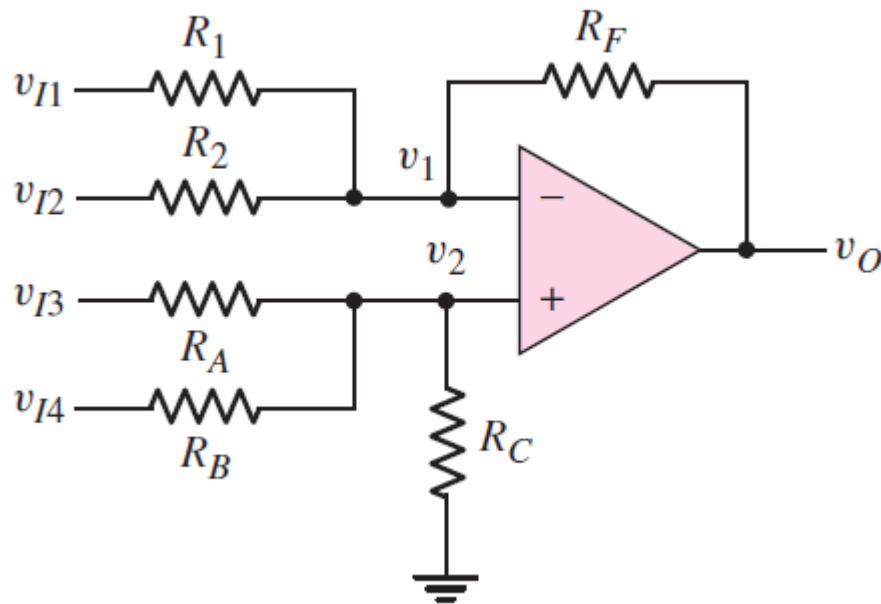
$$v_O = -a_1 v_{I1} - a_2 v_{I2} + a_3 v_{I3} + a_4 v_{I4}$$




Determine the output voltage in terms of input voltages and resistors in the circuit.

Summing Op-Amp Circuit Design

- The output terms due to the inputs given to the inverting terminal v_{I1} and v_{I2} .
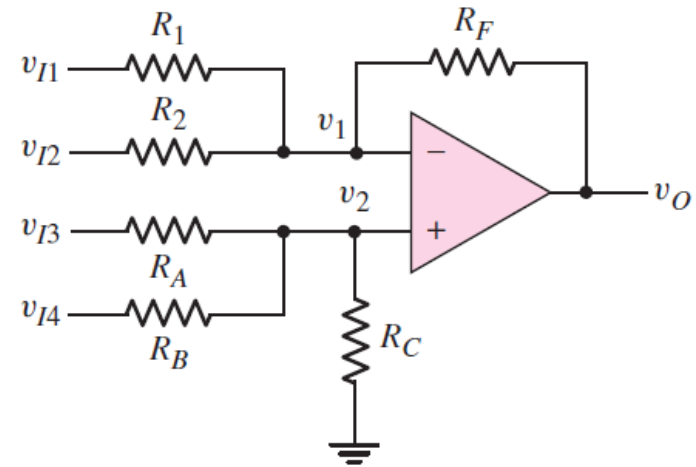
$$v_O(v_{I1}) = -\frac{R_F}{R_1} v_{I1} \quad v_O(v_{I2}) = -\frac{R_F}{R_2} v_{I2}$$



- The output terms due to the inputs given to the non-inverting terminal v_{I3} and v_{I4} .

$$v_2(v_{I3}) = \frac{R_B \parallel R_C}{R_A + R_B \parallel R_C} v_{I3} = v_1(v_{I3})$$

$$v_O(v_{I3}) = \left(1 + \frac{R_F}{R_1 \parallel R_2}\right) v_1(v_{I3}) = \left(1 + \frac{R_F}{R_1 \parallel R_2}\right) \left(\frac{R_B \parallel R_C}{R_A + R_B \parallel R_C}\right) v_{I3}$$

$$v_O(v_{I3}) = \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_A}\right) v_{I3}$$

where,


$$R_N = R_1 \parallel R_2$$

$$R_P = R_A \parallel R_B \parallel R_C$$

Summing Op-Amp Circuit Design

- ✿ The output voltage due to v_{I4} is similarly determined.
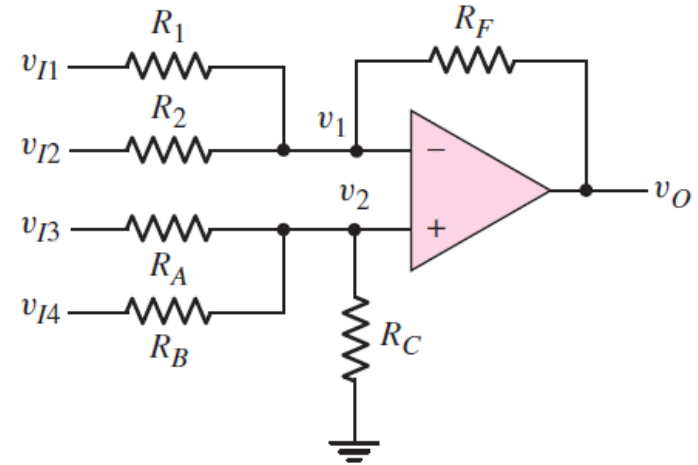
$$v_O(v_{I4}) = \left(1 + \frac{R_F}{R_N}\right) \left(\frac{R_P}{R_B}\right) v_{I4}$$



- ✿ Applying superposition theorem, the total output voltage can be computed as a sum of the individual terms.


$$v_O = -\frac{R_F}{R_1} v_{I1} - \frac{R_F}{R_2} v_{I2} + \left(1 + \frac{R_F}{R_N}\right) \left[\frac{R_P}{R_A} v_{I3} + \frac{R_P}{R_B} v_{I4} \right]$$

Design Example 01: Summing Amplifier

Design a summing op-amp to produce the output

$$v_O = -10v_{I1} - 4v_{I2} + 5v_{I3} + 2v_{I4}$$

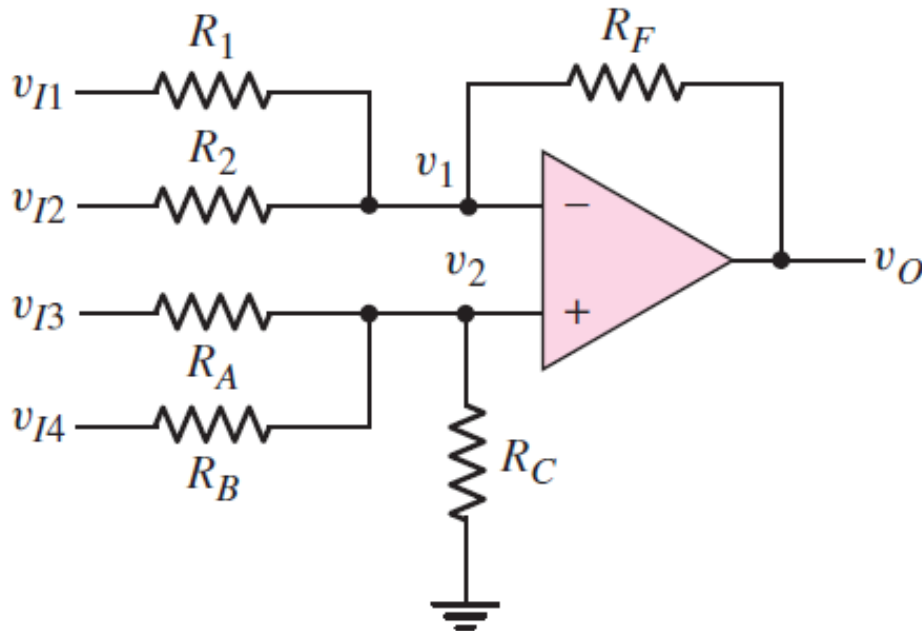The smallest resistor value allowable is $20k\Omega$. Consider the circuit in Figure below.



Design Example 01: Summing Amplifier

Solution:

First we determine the values of resistors R_1 , R_2 , and R_F . (associated with the inverting terms)

$$v_O = -10v_{I1} - 4v_{I2} + 5v_{I3} + 2v_{I4}$$

$$v_O = -\frac{R_F}{R_1}v_{I1} - \frac{R_F}{R_2}v_{I2} + \left(1 + \frac{R_F}{R_N}\right) \left[\frac{R_P}{R_A}v_{I3} + \frac{R_P}{R_B}v_{I4} \right]$$

Then, $\frac{R_F}{R_1} = 10$ and $\frac{R_F}{R_2} = 4$

The resistors R_1 will be the smallest value and set it as $20k\Omega$.

Then, $R_F = 200k\Omega$ and $R_2 = 50k\Omega$

Design Example 01: Summing Amplifier

Solution:

The multiplying factor in the noninverting terms;

$$\left(1 + \frac{R_F}{R_1 \parallel R_2}\right) = \left(1 + \frac{200}{20 \parallel 50}\right) = 15$$

We then need;

$$(15) \left(\frac{R_P}{R_A}\right) = 5 \quad \text{and} \quad (15) \left(\frac{R_P}{R_B}\right) = 2$$


Then;
$$\frac{R_B}{R_A} = \frac{5}{2}$$

If we choose $R_A = 80k\Omega$, then $R_B = 200k\Omega$, $R_P = 26.67k\Omega$, and R_C becomes $R_C = 50k\Omega$.

Difference Amplifier and Bridge Circuit Design

Resistance R_3 represents the transducer, and parameter δ is the deviation of R_3 from R_2 due to the input response of the transducer.

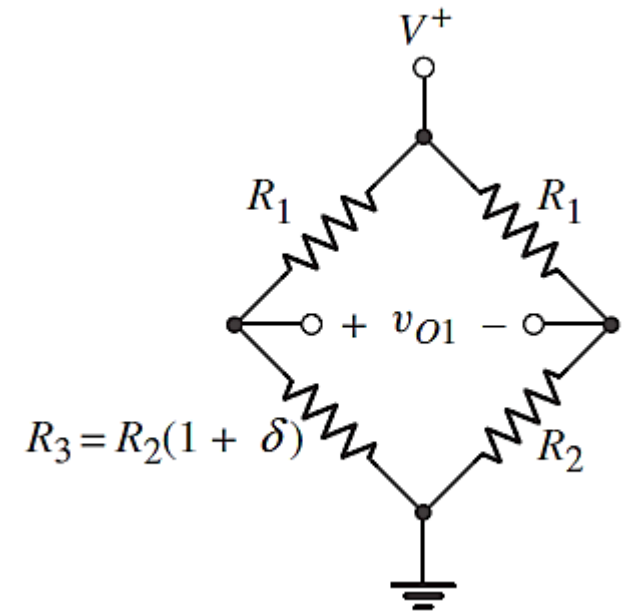The output voltage v_{O1} is a measure of δ . If v_{O1} is an open-circuit voltage;



Bridge Circuit

$$v_{O1} = \left[\frac{R_2(1 + \delta)}{R_2(1 + \delta) + R_1} - \frac{R_2}{R_1 + R_2} \right] V^+$$

Which can be reduced to;

$$v_{O1} = \delta \left(\frac{R_1 \parallel R_2}{R_1 + R_2} \right) V^+$$

Ex. 02: Difference Amplifier and Bridge Circuit Design

Design an amplifier system that will produce an output voltage of $\pm 5V$ when the resistance R_3 deviates by $\pm 1\%$ from the value of R_2 . This would occur, for example, in a system where R_3 is a thermistor whose resistance is given by;

$$R_3 = 200 \left[1 + \frac{(0.040)(T - 300)}{300} \right] \text{ k}\Omega$$

where T is the absolute temperature. For R_3 to vary by $\pm 1\%$ means the temperature is in the range $225 \leq T \leq 375K$. Consider biasing the bridge circuit at $V^+ = 7.5V$ using a $5.6V$ Zener diode. Assume $\pm 10V$ is available for biasing the op-amp and reference voltage source, and that $R_1 = R_2 = 200k\Omega$.

Ex. 02: Difference Amplifier and Bridge Circuit Design

Solution:

With $R_1 = R_2$,
$$v_{O1} = \delta \left(\frac{R_1 \parallel R_2}{R_1 + R_2} \right) V^+ \quad \Rightarrow \quad v_{O1} = \left(\frac{\delta}{4} \right) V^+$$

For $V^+ = 7.5 \text{ V}$ and $\delta = 0.01$ (1%), the maximum output voltage,

$$v_{O1} = 0.01875 \text{ V}$$

If the output is to be +5 V, the gain of the amplifier must be $\frac{5}{0.01875} = 266.7$

Ex. 02: Difference Amplifier and Bridge Circuit Design


☼ Let's consider the instrumentation amplifier below; the output voltage:

$$v_O = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1} \right) (v_{I2} - v_{I1})$$

$$\frac{v_O}{v_{O1}} = \frac{R'_4}{R'_3} \left(1 + \frac{2R'_2}{R'_1} \right) = 266.7$$

We would like the ratios R'_4/R'_3 and R'_2/R'_1 to be the same order of magnitude.

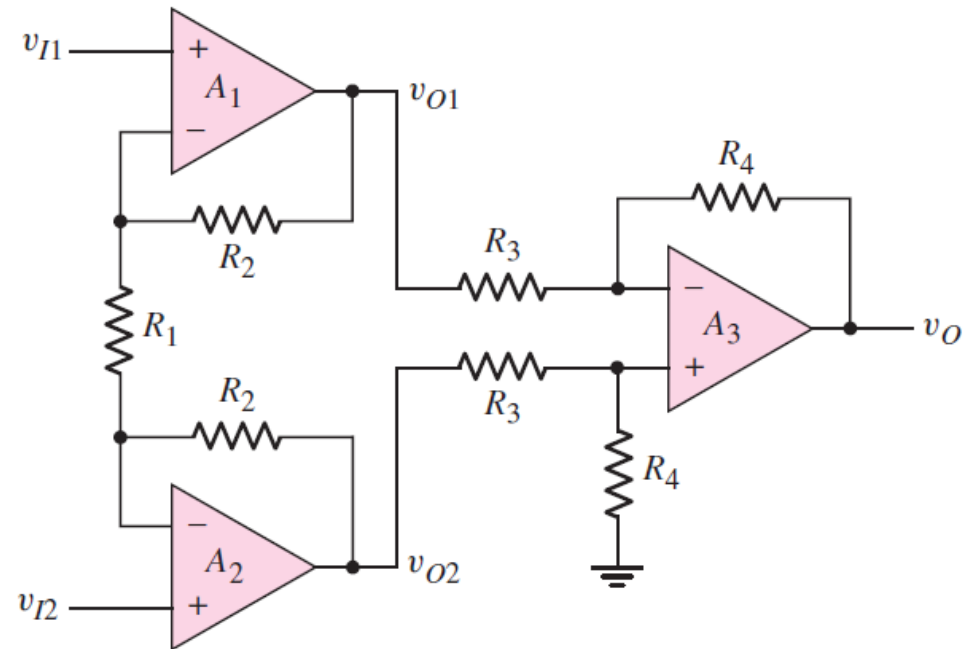
If set $R'_3 = 15 \text{ k}\Omega$ and $R'_4 = 187 \text{ k}\Omega$, then $R'_4/R'_3 = 12.467$ and $R'_2/R'_1 = 10.195$.



If set $R'_2 = 200 \text{ k}\Omega$ then $R'_1 = 19.62 \text{ k}\Omega$

Ex. 02: Difference Amplifier and Bridge Circuit Design

✿ The complete design of the instrumentation amplifier:

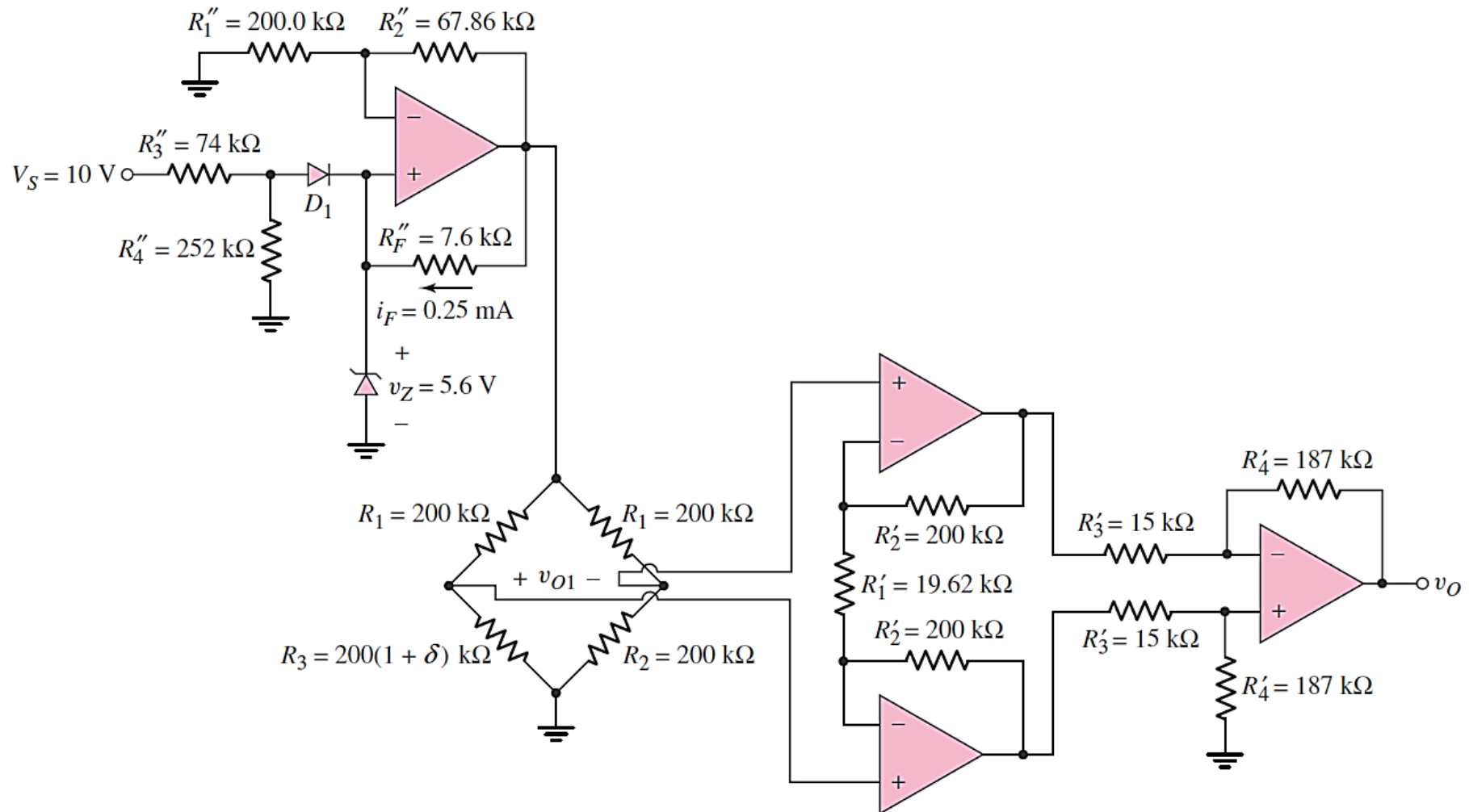


Ex. 03 : Current-to-Voltage Converter

A current-to-voltage converter is shown in Figure below. The current source has a finite output resistance R_S , and the op-amp has a finite open-loop differential gain A_{od} .

a) Show that the input resistance is given by:
$$R_{in} = \frac{R_F}{1 + A_{od}}$$

b) If $R_F = 10k\Omega$ and $A_{od} = 1000$, determine the range of R_S such that the output voltage deviates from its ideal value by less than 1 percent.

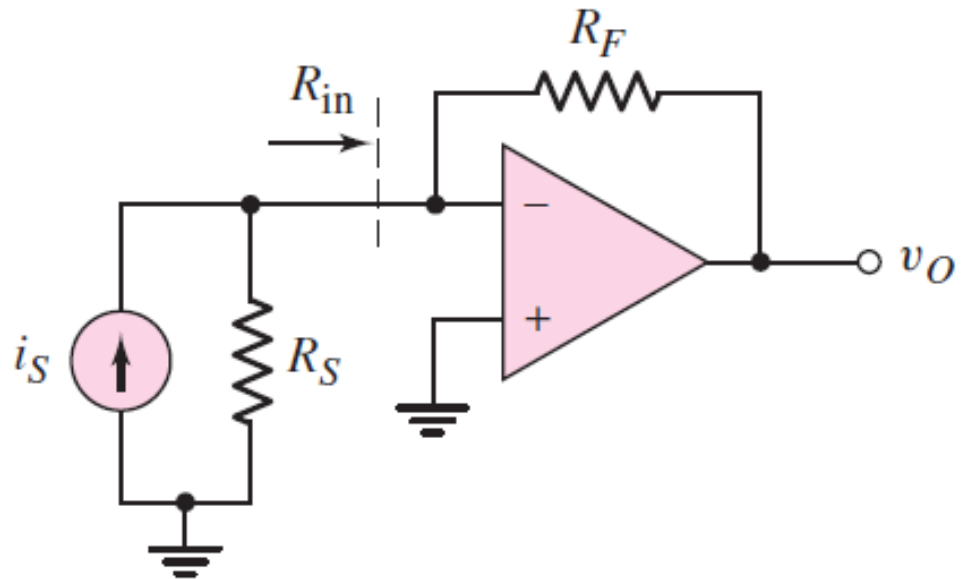

Ex. 04 : Current-to-Voltage Converter

Figure below shows a phototransistor that converts light intensity into an output current. The transistor must be biased as shown. The transistor output versus input characteristics are shown. Design a current-to-voltage converter to produce an output voltage between 0 and 8 V for an input light intensity between 0 and 20 mW/cm^2 . Power supplies of +10V and -10V are available.

